

Logic Design

lecture 06 $\leadsto$ Binary logic

$\Downarrow$

Boolean Algebra

Boolean algebra $\Rightarrow$ Deals with variables that take on two discrete values and operations that assume logical meaning

true — false

yes — No

1, 0

So variable A in binary logic may be 1 or zero

Logical operation $\Rightarrow$ AND — OR — NOT


AND $X \cdot Y \Rightarrow XY \Rightarrow X \text{ and } Y$

OR $X + Y \Rightarrow X \text{ OR } Y$

NOT $\overline{X} \Rightarrow X' \Rightarrow X \text{ Complement}$

NOT

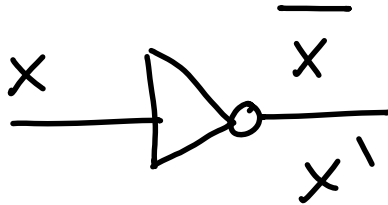- Complement $\Rightarrow$ Negate $\Rightarrow$ Inverter
- Single input
- $\overline{X} \Rightarrow X'$




X	$\overline{X}$
0	1
1	0

$\Rightarrow$ Truth table

AND

- Operation to check if two conditions are met
- two inputs or more
- Outputs 1 if and only if both input are 1


X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

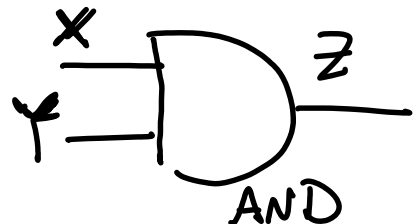

- $X \cdot Y \Rightarrow XY \Rightarrow X \text{ and } Y$

OR

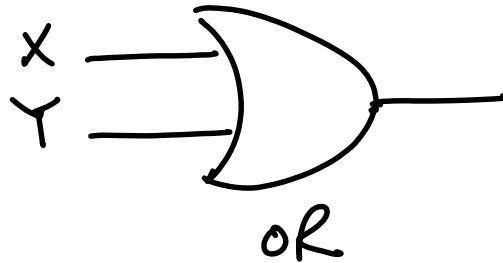- Operation to check if
at least one condition is met
- may be two inputs or more
- outputs 1 if any input is 1
- $X + Y$



X	Y	OR
0	0	0
0	1	1
1	0	1
1	1	1

To conclude

X	Y	AND $X \cdot Y$	OR $X + Y$	NOT X	NOT Y
0	0	0	0	1	1
0	1	0	1	1	0
1	0	0	1	0	1
1	1	1	1	0	0

Logic Gates

Circuits that operate on one or more input signals to produce an output signals

- AND
- OR
- NOT


Electrical
Signals
Voltage
Current

Range of electrical Signals



+ TTL + 7400
7402
74 —→

Other two-input
gates

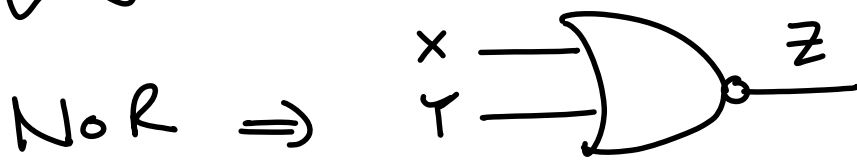


X	Y	$X+Y$	Nor $\overline{X+Y}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

$\Rightarrow Z = \overline{X+Y}$

Existence of 1 $\Rightarrow$ 0 output

NAND

X	Y	AND $X \cdot Y$	NAND $\overline{XY}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

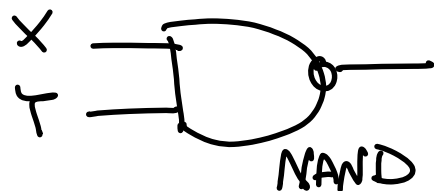


$$Z = \overline{XY}$$

Existence of 0 lead to 1

XOR

X	Y	XOR
0	0	0
0	1	1
1	0	1
1	1	0


Exclusive
OR

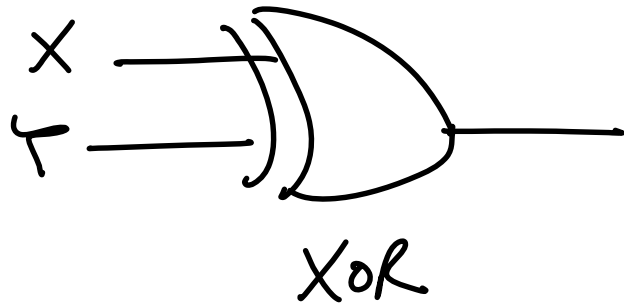

$$Z = X \oplus Y$$

if No. of 1 in input is odd, the output
is 1

XNOR

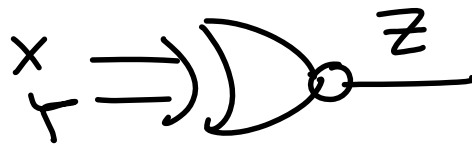


$$Z = \overline{X \oplus Y}$$

$$Z = X \odot Y$$

X	Y	XNOR
0	0	1
0	1	0
1	0	0
1	1	1

Gates with more than
2 inputs

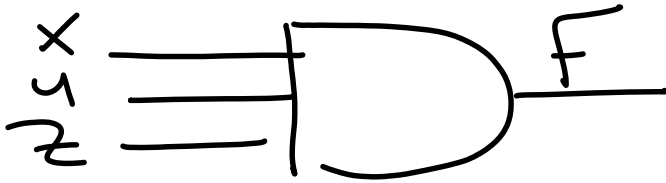

$$F = xyz$$


$$= x \cdot y \cdot z$$

x	y	z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Ex

Truth table for three input OR

x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

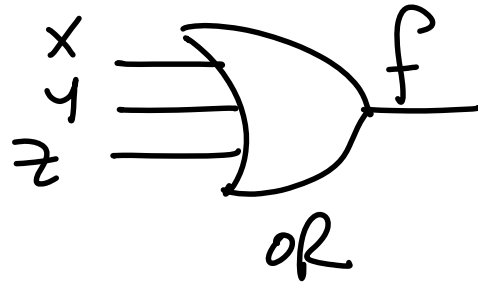

$$f = x + y + z$$

Boolean Algebra

$$\overline{0} = 1 \quad || \quad A + 1 = 1 \quad || \quad A + \overline{A} = 1$$

$$\overline{1} = 0 \quad || \quad A + A = A \quad || \quad A + 0 = A$$

$$\bullet \overline{\overline{A}} = A \quad \bullet A \cdot 0 = 0 \quad \bullet A \cdot 1 = A$$

$$\bullet A \cdot A = A \quad \bullet A \cdot \overline{A} = 0$$

$$\bullet A(B + C) = AB + AC$$

Ex Sketch Truth table, logic diagram

$$F = x + \bar{y}z$$

$$\begin{aligned} F &= 0 + \bar{0} \cdot 0 \\ &= 0 + 1 \cdot 0 \\ &= 0 + 0 \\ &= 0 \end{aligned}$$


x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

0 0 1
x y z

$$F = x + \bar{y}z$$


$$= 0 + \bar{0} \cdot 1$$

$$= 0 + 1 \cdot 1 = 0 + 1 = 1$$

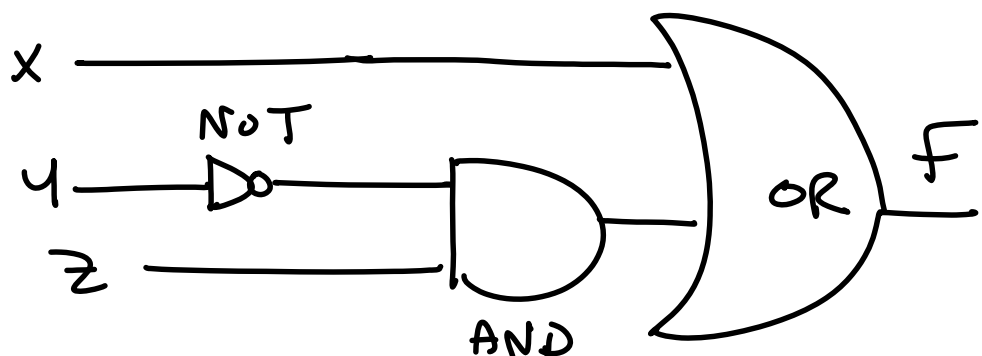


Note

→ this function is an OR

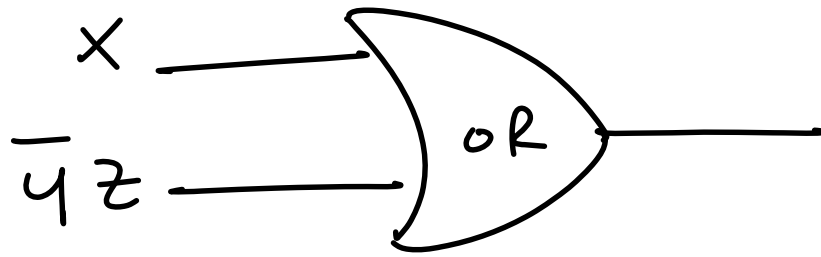

• Results in 1 if one side is 1

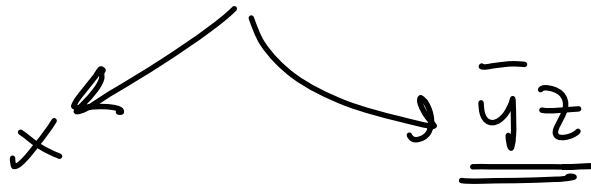

if x is
1 $\Rightarrow$ output
is 1

this is an AND
gate

↓ continue