

Agenda

- Product

- Sum

- minterm

- maxterm

- Sum-of-product

- product-of-sum

Ex

Design a majority circuit that produce 1 if more half the inputs are all 1. Design for 3-inputs

Sol.

x	y	z	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$\Rightarrow f = \bar{x}yz + x\bar{y}z + x\bar{y}\bar{z} + x\bar{y}z$$

$$\begin{aligned}
 f &= \bar{x}yz + x\bar{y}z + xy(z + \bar{z}) \\
 &= \bar{x}yz + x\bar{y}z + xy \\
 &= z(x \oplus y) + xy
 \end{aligned}$$

Canonical forms

Product: the AND of one or more literals is called a product or an implicit, like $\bar{A}B$, AC , $B\bar{C}$ are all implicants for a function of three variables

minterm: is a product involving all of the inputs to the function

Ex $A\bar{B}\bar{C}$ is a minterm for a function of three variable A, B, C

$\overline{A}B$ is a product, Not a minterm
because it does not involve C

Sum : The OR of one or more literals
is called a sum. like $A+B$,

$$\overline{A}+B, A+B+\overline{C}$$

maxterm : is a sum involving all of
the inputs to the function

Ex $A+\overline{B}+C$ is a maxterm for
a function of the three variables
 A, B , and C

<u>Minterm</u>				<u>Maxterm</u>	
x	y	term	designation	term	designation
0	0	$\overline{x}\overline{y}$	m_0	$x+y$	M_0
0	1	$\overline{x}y$	m_1	$x+\overline{y}$	M_1
1	0	$x\overline{y}$	m_2	$\overline{x}+y$	M_2
1	1	xy	m_3	$\overline{x}+\overline{y}$	M_3

For three
Variables

x	y	z	term		term	
0	0	0	$\bar{x}\bar{y}\bar{z}$	m ₀	$x+y+z$	m ₀
0	0	1	$\bar{x}\bar{y}z$	m ₁	$x+y+\bar{z}$	m ₁
0	1	0	$\bar{x}y\bar{z}$	m ₂	$x+\bar{y}+z$	m ₂
0	1	1	$\bar{x}yz$	m ₃	$x+\bar{y}+\bar{z}$	m ₃
1	0	0	$x\bar{y}\bar{z}$	m ₄	$\bar{x}+y+z$	m ₄
1	0	1	$x\bar{y}z$	m ₅	$\bar{x}+y+\bar{z}$	m ₅
1	1	0	$xy\bar{z}$	m ₆	$\bar{x}+\bar{y}+z$	m ₆
1	1	1	xyz	m ₇	$\bar{x}+\bar{y}+\bar{z}$	m ₇

Sum-of-product SOP

We can write a boolean function for any truth table by summing each of the minterms for which the output, Y , is true

Ex

A	B	Y	minterm
0	0	0	$\bar{A}\bar{B}$
0	1	1	$\bar{A}B$
1	0	0	$A\bar{B}$
1	1	0	AB

← minterm for which Y is equal to 1

$$\therefore Y = \bar{A}B$$

Ex

A	B	Y	minterm
0	0	0	$\bar{A}\bar{B}$
0	1	1	$\bar{A}B$
1	0	0	$A\bar{B}$
1	1	1	AB

$$Y = \bar{A}B + AB = B$$

Ex

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

$$Y = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}C + AB\bar{C}$$

Ex Express the output of 3-input majority gate as SOP term.

<u>Sol</u>	A	B	C	F	minterm	Designation
	0	0	0	0	$\bar{A}\bar{B}\bar{C}$	m ₀
	0	0	1	0	$\bar{A}\bar{B}C$	m ₁
	0	1	0	0	$\bar{A}B\bar{C}$	m ₂
→	0	1	1	1	$\bar{A}BC$	m ₃
	1	0	0	0	$A\bar{B}\bar{C}$	m ₄
→	1	0	1	1	$A\bar{B}C$	m ₅
→	1	1	0	1	$AB\bar{C}$	m ₆
→	1	1	1	1	ABC	m ₇

$$F = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

$$F = m_3 + m_5 + m_6 + m_7$$

$$F = \sum (3, 5, 6, 7)$$

think in it
as

011

↓

$\bar{A}BC$

101

$A\bar{B}C$

Ex

find the sum-of-product, and product-of-sum of the truth table shown below

A	B	Y
0	0	0
0	1	0
→ 1	0	1
→ 1	1	1

$$Y = A\bar{B} + AB$$

$$Y = m_2 + m_3$$

$$Y = \sum (2, 3)$$

$$Y \text{ as SOP} = \sum (2, 3)$$

$$Y = (A + B)(A + \bar{B}) \Rightarrow \text{POS}$$

$$\begin{aligned} Y &= A + A\bar{B} + AB \\ &= A(1 + B + \bar{B}) \end{aligned}$$

$$Y = A$$

$$\begin{aligned} Y &= \overline{K}(M_0, M_1) \\ &= \overline{K}(0, 1) \end{aligned}$$

Ex Find the SOP of the truth table shown below

x	y	z	f ₁	f ₂
0	0	0	0	1
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\Rightarrow f_1 = \sum (1, 4, 7)$$

$$\Rightarrow f_2 = \sum (0, 3, 5, 6, 7)$$

$$\therefore f_1(x, y, z) = \sum (1, 4, 7)$$

001 100 111

$$f_1 = \bar{x}\bar{y}z + x\bar{y}\bar{z} + xy z$$

$$\therefore f_2(x, y, z) = \sum (0, 3, 5, 6, 7)$$

$$f_2 = \bar{x}\bar{y}\bar{z} + \bar{x}y\bar{z} + x\bar{y}\bar{z} + xy\bar{z} + xy z$$

product-of-Sum : POS

We can write a boolean equation for any circuit directly from truth table as the AND of each of the maxterms which the output is false

Ex

	A	B	C	Y	
→	0	0	0	0	M_0
	0	0	1	1	
	0	1	0	1	
	0	1	1	1	
→	1	0	0	0	M_4
	1	0	1	0	M_5
	1	1	0	1	
	1	1	1	0	M_7

$$Y = M_0 M_4 M_5 M_7$$

$$= \overline{A}(0, 4, 5, 7)$$

000 100 101 111

$$Y = (A+B+C)(\bar{A}+B+C)(\bar{A}+B+\bar{C})(\bar{A}+\bar{B}+\bar{C})$$

Ex

A	B	Y
0	0	0
→ 0	1	1
→ 1	0	1
→ 1	1	1

Y as SOP

$$\hookrightarrow = \sum (1, 2, 3)$$

$$= \bar{A}B + A\bar{B} + AB$$

$$= \bar{A}B + A(\bar{B} + B)$$

$$= \bar{A}B + A$$

$$= (A + \bar{A})(A + B)$$

$$= A + B$$

A	B	Y
→ 0	0	0
0	1	1
1	0	1
1	1	1

Y as POS

$$\hookrightarrow = \prod (0)$$

$$= A + B$$

Ex Express the truth table below in product-of-Sum and Sum-of-product, prove that, they are equivalent

A	B	f
0	0	0
0	1	1
1	0	0
1	1	1

$$\begin{aligned}F &= \sum (1, 3) \\&= \bar{A}B + AB \\&= B\end{aligned}$$


$$\begin{aligned}F &= \prod (0, 2) = (A+B)(\bar{A}+B) \\&= AB + \bar{A}B + B \\&= B(A + \bar{A} + 1) \\&= B\end{aligned}$$

Ex implement the truth table below

x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$$\Rightarrow f = \sum(1, 5, 7)$$
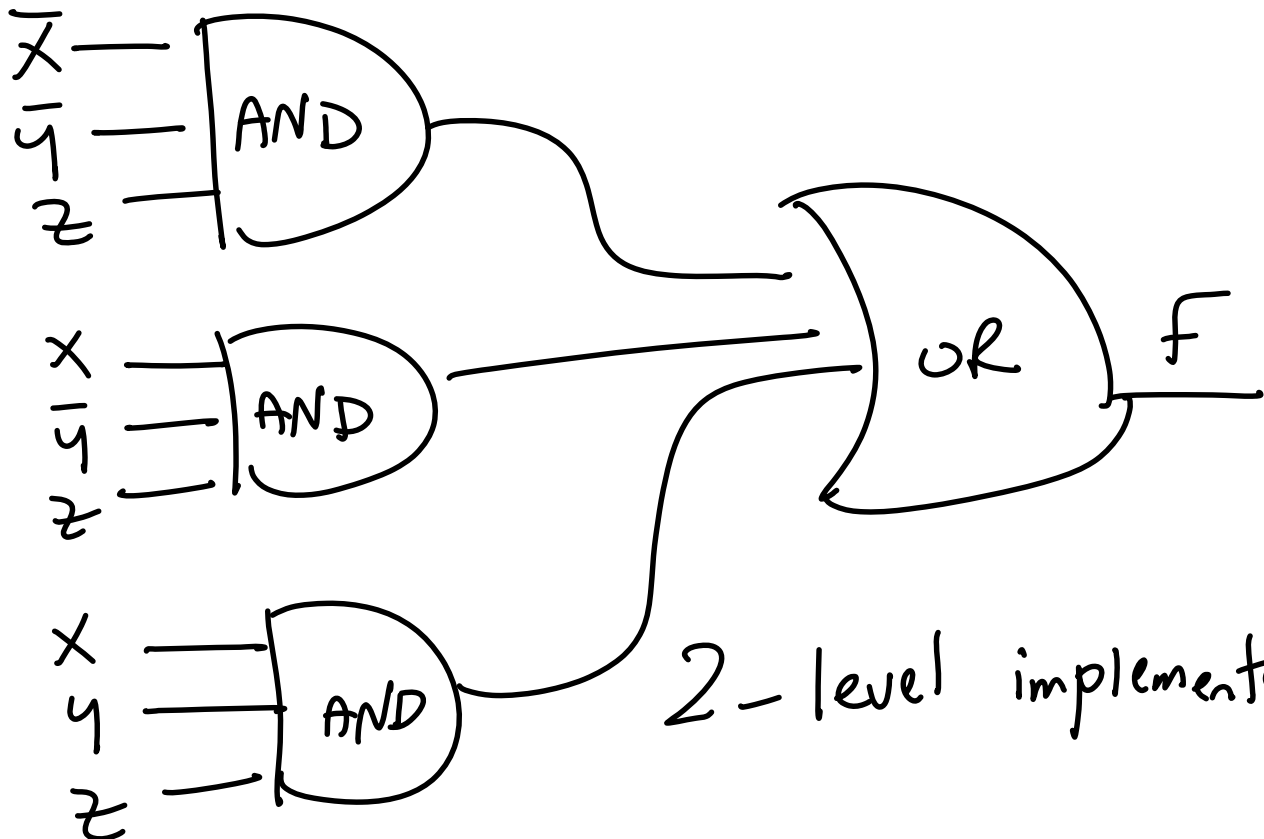
$$f = \bar{x}\bar{y}z + x\bar{y}z + xy z$$



2-level implementation


Ex write down the product-of-sum form of the truth table shown below, implement this function.

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$\Rightarrow Y = \prod (1, 2, 5, 6)$$

001 010 101 110
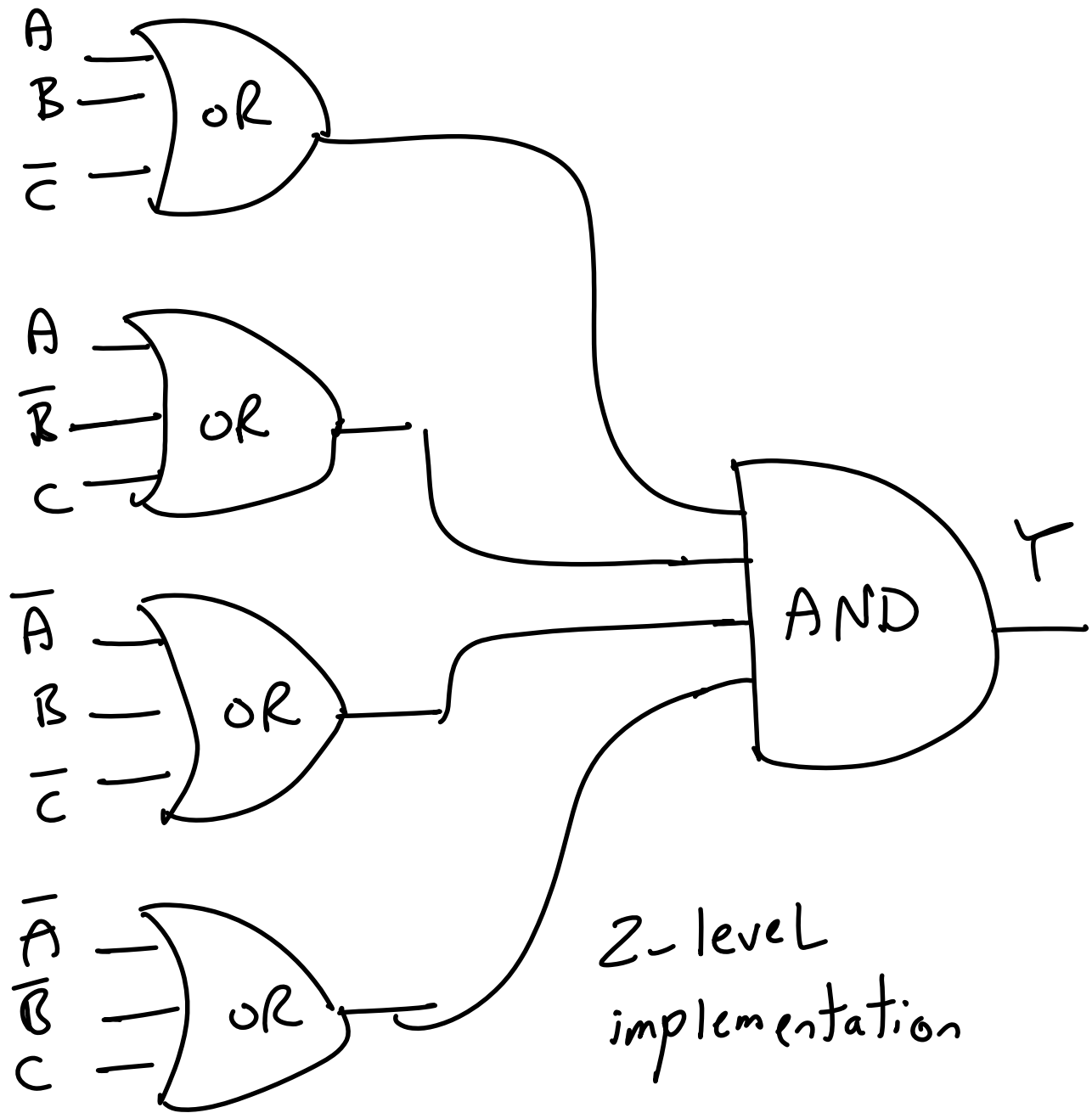
$$Y = (A + B + \bar{C})(A + \bar{B} + C)(\bar{A} + B + \bar{C})(\bar{A} + \bar{B} + C)$$





Ex write down SOP, and POS of the truth table shown below, implement them

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

$$\Rightarrow Y = \sum(0) = \bar{A}\bar{B}$$

$$Y = \prod(1,2,3)$$
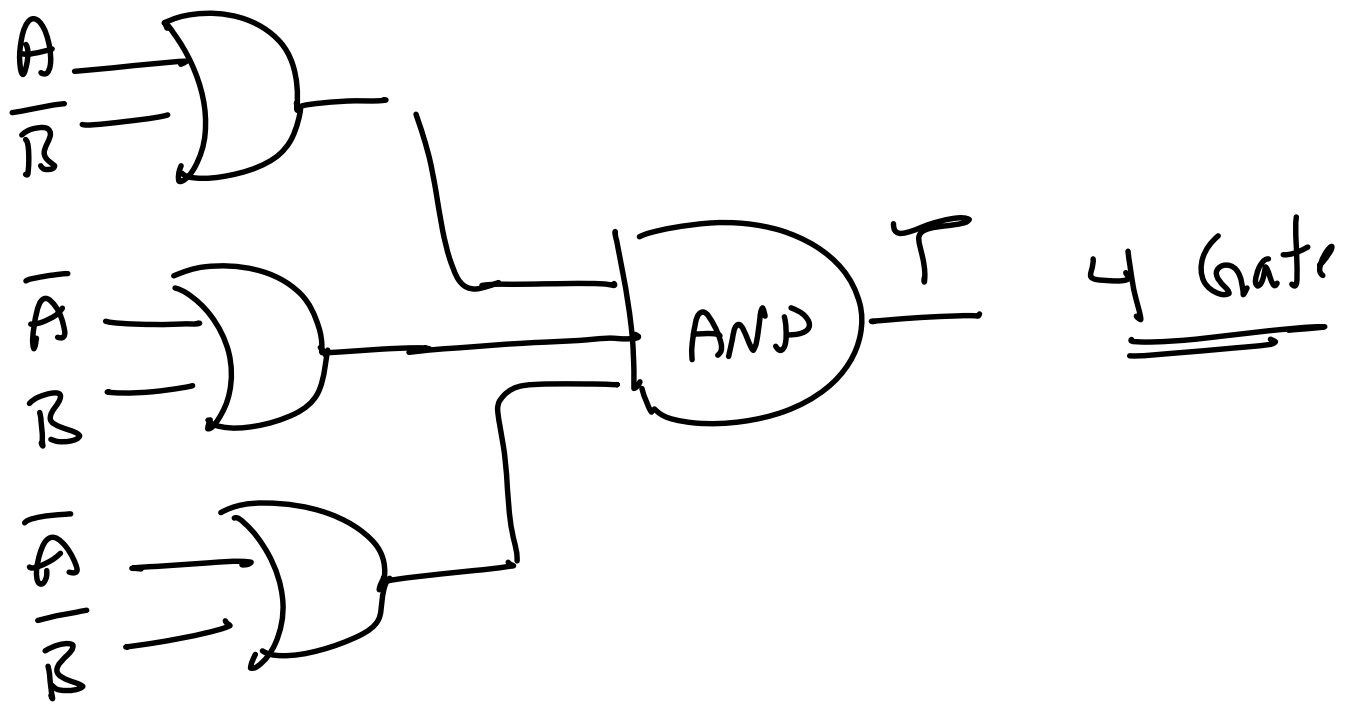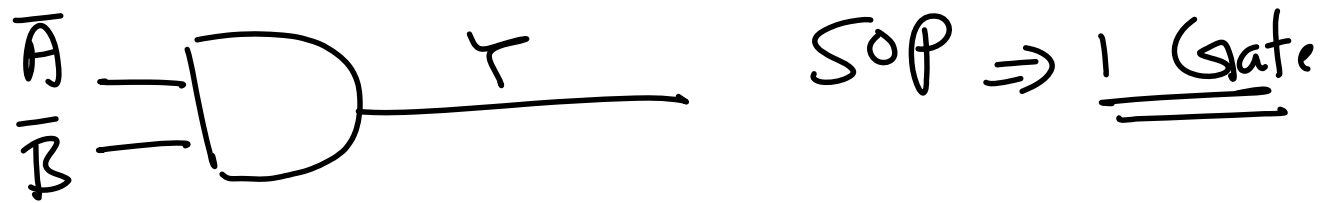
$$T \Rightarrow \text{POS} = (A + \bar{B})(\bar{A} + B)(\bar{A} + \bar{B})$$




unfortunately, SOP, and POS does not necessarily produce the simplest equation, later we will come to that point




How to implement using fewer gates

NAND - NOR as universal Gate


NOT using NAND

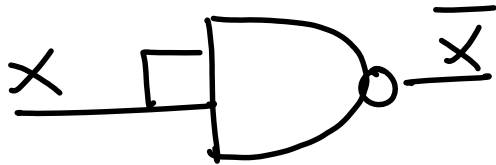

AND using NAND

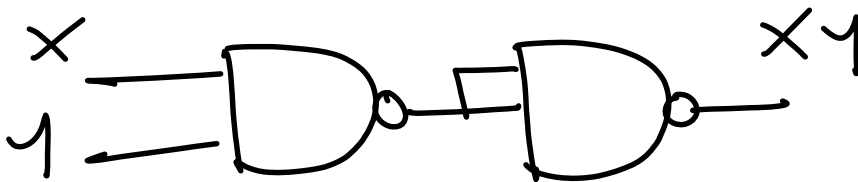

OR using NAND

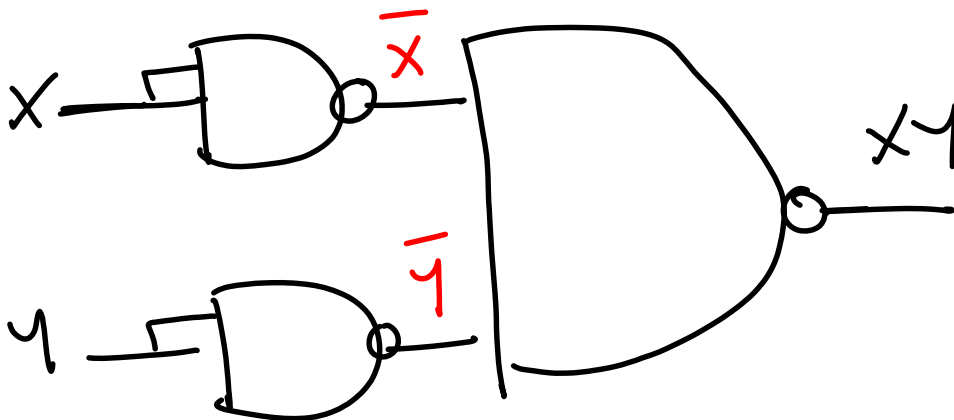

NOR as universal
Gate

$\Rightarrow$ Report

Ex $F = x + \bar{y}z$, is it in canonical form?

Sol No, but we can convert

$\swarrow$ mathematically $\searrow$ by truth table

$$F = x(y + \bar{y})(z + \bar{z}) + (x + \bar{x})\bar{y}z$$

$$= xyz + xy\bar{z} + x\bar{y}z + x\bar{y}\bar{z}$$

$$+ x\bar{y}z + \bar{x}\bar{y}z$$

$$= \sum(1, 4, 5, 6, 7)$$

by truth table

$$x + \bar{y}z$$

x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$f = \sum(1, 4, 5, 6, 7)$$

Ex Find the product-of-sum of

$$F = xy + \bar{x}z$$

(1) mathematically

$$F = (xy + \bar{x})(xy + z)$$

$$= (x + \bar{x})(\bar{x} + y)(x + z)(y + z)$$

$$= (\bar{x} + y)(x + z)(y + z)$$

$$= (\bar{x} + y + z\bar{z})(x + z + y\bar{y})(y + z + x\bar{x})$$

$$F = (\bar{x} + y + z)(\bar{x} + y + \bar{z})$$

$$(x + y + z)(x + \bar{y} + z)$$

$$(x + y + z)(\bar{x} + y + z)$$

$$F = \pi(4, 5, 0, 2, 0, 4)$$

$$f = \pi(0, 2, 4, 5)$$

② by truth table $\Rightarrow f = xy + \bar{x}z$

x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$f = \pi(0, 2, 4, 5)$$

Conversion between Canonical forms

$$f(x, y, z) = \sum (1, 4, 5, 6, 7)$$

$\Downarrow$

$$f(x, y, z) = \prod (0, 2, 3)$$

Ex Derive the truth table, and obtain sum of product and product of sum of

$$f = \bar{x} + yz$$

x	y	z	f
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

$$f = \sum (0, 1, 2, 3, 7)$$

$$f = \prod (4, 5, 6)$$