

Ex:

Design a digital circuit that accepts a 3-bit number and produce the square of that no.

Solution

maximum number that can be represented in 3-bit is $7_{10} \Rightarrow$ the square of 7_{10} is $49_{10} \Rightarrow$ need at least 6-bit, namely, $49 \Rightarrow (110001)_2$

A_2	A_1	A_0	C_5	C_4	C_3	C_2	C_1	C_0
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1
0	1	0	0	0	0	1	0	0
0	1	1	0	0	1	0	0	1
1	0	0	0	1	0	0	0	0
1	0	1	0	1	1	0	0	1
1	1	0	1	0	0	1	0	0
1	1	1	1	1	0	0	0	1

C_0

$A_2 \backslash A_1 A_0$		00	01	11	10
0			1	1	
1			1	1	

$$C_0 = A_0$$

C_1

$A_2 \backslash A_1 A_0$		00	01	11	10
0					
1					

$$C_1 = 0$$

C_2

$A_2 \backslash A_1 A_0$		00	01	11	10
0					1
1					1

$$C_2 = A_1 \bar{A}_0$$

C_3

$A_2 \backslash A_1 A_0$		00	01	11	10
0				1	
1			1		

$$C_3 = \bar{A}_2 A_1 A_0 + A_2 \bar{A}_1 A_0$$

C_4

$A_2 \backslash A_1 A_0$		00	01	11	10
0					
1	1	1	1		

$$C_4 = A_2 \bar{A}_1 + A_2 A_0$$

C_5

$A_2 \backslash A_1 A_0$		00	01	11	10
0					
1				1	1

$$C_5 = A_2 A_1$$

$$C_0 = A_0$$

$$C_1 = 0$$


$$C_2 = A_1 \bar{A}_0$$

$$C_3 = \bar{A}_2 A_1 A_0 + A_2 \bar{A}_1 A_0$$

$$= A_0 (A_2 \oplus A_1)$$

$$C_4 = A_2 \bar{A}_1 + A_2 A_0$$

$$C_5 = A_2 A_1$$

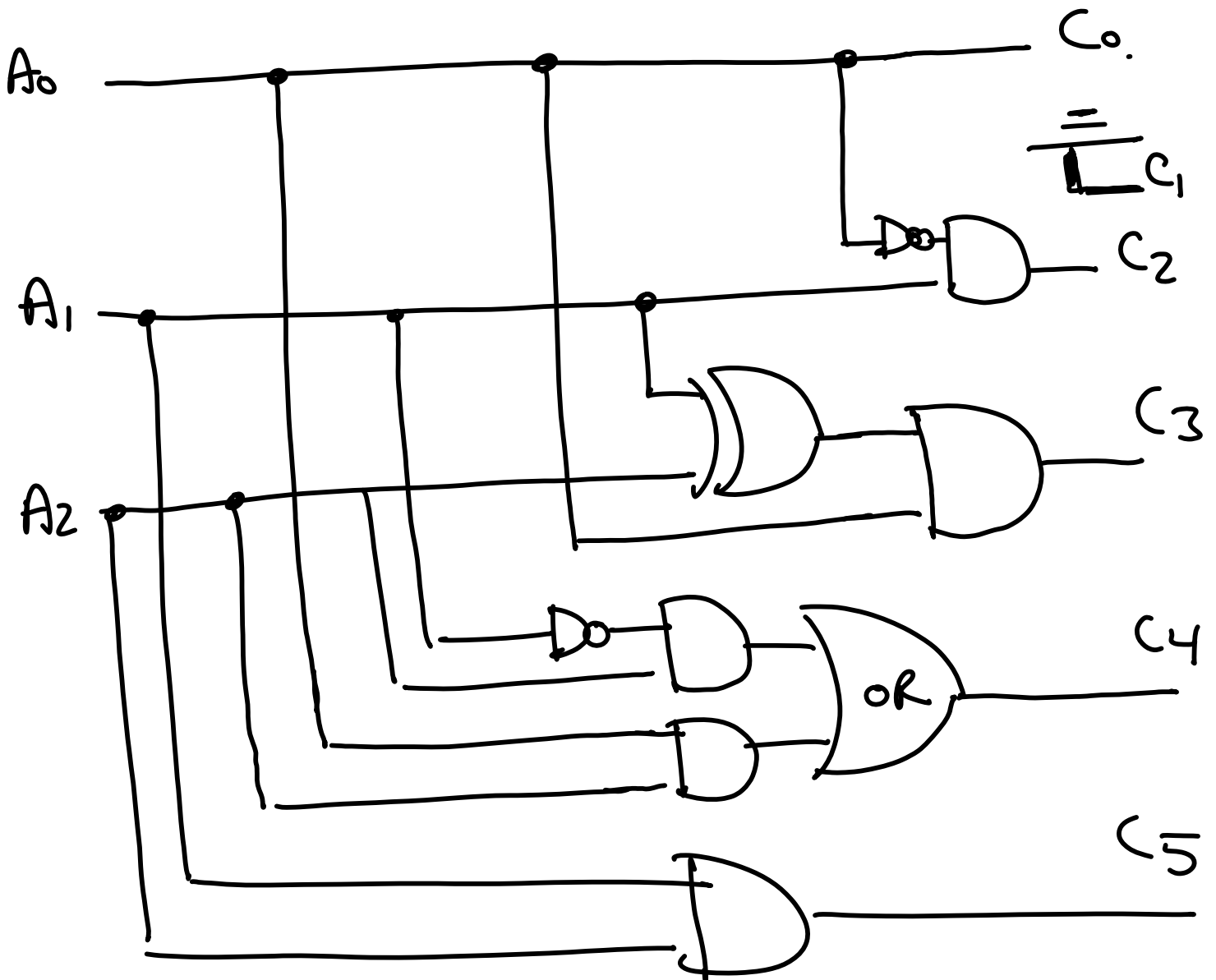

Ex

Design a digital circuit that can add two bits in addition to one bit called carry

x	y	z	c	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$s = \sum (1, 2, 4, 7)$$


$$c = \sum (3, 5, 6, 7)$$

x \ yz	00	01	11	10
0		1		1
1	1		1	

$$s = x \oplus (y \oplus z)$$

x \ yz	00	01	11	10
0			1	
1		1	1	1

$$c = xz + xy + yz$$

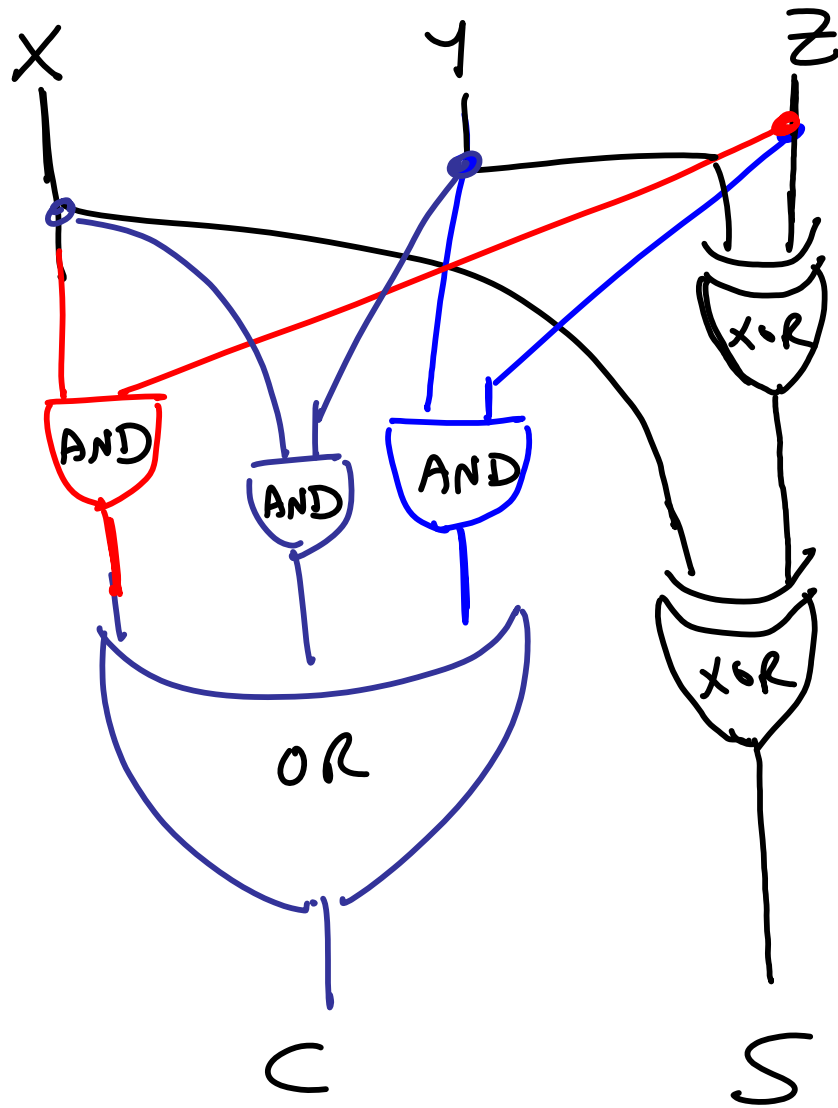

Don't care conditions

↳ where some input variable combinations are not allowed

• in BCD, there are six invalid combinations: 1010, 1011, 1100, 1101, 1110, 1111

- Since these combinations are not allowed — will never occur in an application involving the BCD.



they can be treated as
don't care

→ with respect to
their effect on the
Output

→ You may consider "don't care" terms
either a 1 or 0 — it really does
not matter since they will never
occur — advantage to Karnaugh
map

Ex

Design a digital circuit that has a 1 output only when the BCD code for 2 or 6 is present on the inputs

A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

1 or 0

↑

↑

↑

↑

↑

AB \ CD	00	01	11	10
00				1
01				1
11				
10				

Don't care
as 0

$$\Rightarrow f = \bar{A}C\bar{D}$$

AB \ CD	00	01	11	10
00				1
01				1
11	1	1	1	1
10			1	1

Don't care
as 1


$$f = \bar{C}\bar{D} + AB + AC$$

AB \ CD	00	01	11	10
00				1
01				1
11	X	X	X	X
10			X	X


Don't care
as Don't care

$$f = C\bar{D}$$

Ex 7-segment Display

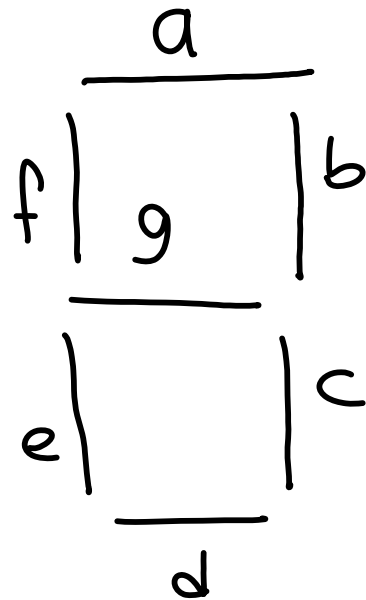

A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	1
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

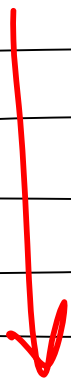

Do not care

$$a = \sum (0, 2, 3, 5, 6, 7, 8, 9)$$

$$b = \sum (0, 1, 2, 3, 4, 7, 8, 9)$$

$$c = \sum (0, 1, 3, 4, 5, 6, 7, 8, 9)$$

$$d = \sum (0, 2, 3, 5, 6, 8, 9)$$

$$e = \sum (0, 2, 6, 8)$$

$$f = \sum (0, 4, 5, 6, 8, 9)$$

$$g = \sum (2, 3, 4, 5, 6, 7, 8, 9)$$

AB \ CD	00	01	11	10
00	1		1	1
01		1	1	1
11	x	x	x	x
10	1	1	x	x

$$a = \overline{B} \overline{D} + BD + C + A$$

Quiz

- Draw the logic diagram for the segment a
- use karnaugh map to get simplified expression for other segments
- Draw logic diagram



(b)

AB \ CD	00	01	11	10
00				
01				
11	X	X	X	X
10			X	X

(c)

AB \ CD	00	01	11	10
00				
01				
11	X	X	X	X
10			X	X

(d)

AB \ CD	00	01	11	10
00				
01				
11	X	X	X	X
10			X	X

(e)

AB \ CD	00	01	11	10
00				
01				
11	X	X	X	X
10			X	X

(f)

AB \ CD	00	01	11	10
00				
01				
11	X	X	X	X
10			X	X

(g)

AB \ CD	00	01	11	10
00				
01				
11	X	X	X	X
10			X	X

Report

- use MultiSim
- use Proteus
- Getting started $\Rightarrow$ MultiSim
- Getting started $\Rightarrow$ Proteus

Ex

Develop a circuit that converts a BCD digit into Excess-3 code

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

(W)

AB \ CD	00	01	11	10
00				
01		1	1	1
11	X	X	X	X
10	1	1	X	X

(X)

AB \ CD	00	01	11	10
00		1	1	1
01	1			
11	X	X	X	X
10		1	X	X

$$W = A + BD + BC$$

$$X = B\bar{C}\bar{D} + \bar{B}D + \bar{B}C$$

④

AB \ CD	00	01	11	10
00	1		1	
01	1		1	
11	X	X	X	X
10	1		X	X

$$Y = \bar{C}\bar{D} + CD$$

⑤

AB \ CD	00	01	11	10
00	1			1
01	1			1
11	X	X	X	X
10	1		X	X


$$Z = \bar{D}$$

Report

Design a BCD to Gray Code
converter

Ex

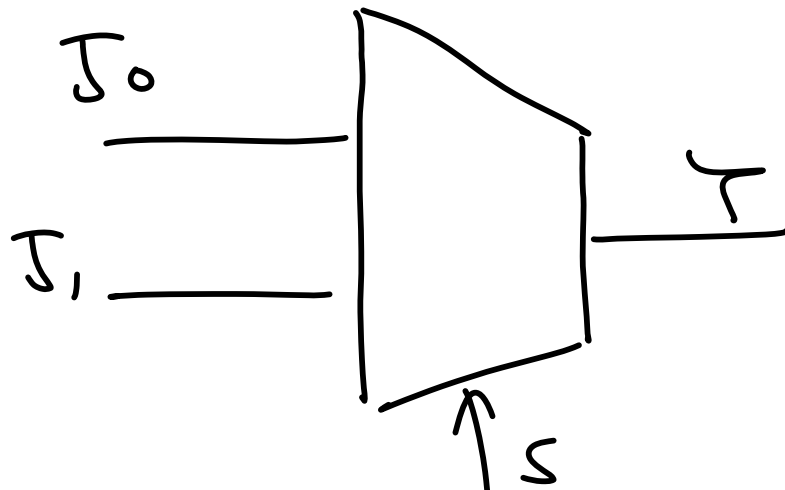Design a digital circuit that produce
Y output equal to I_0 if selection
bit $S = 0$. Y equal to I_1 if
 $S = 1$



$$Y = \begin{cases} I_0 & S = 0 \\ I_1 & S = 1 \end{cases}$$