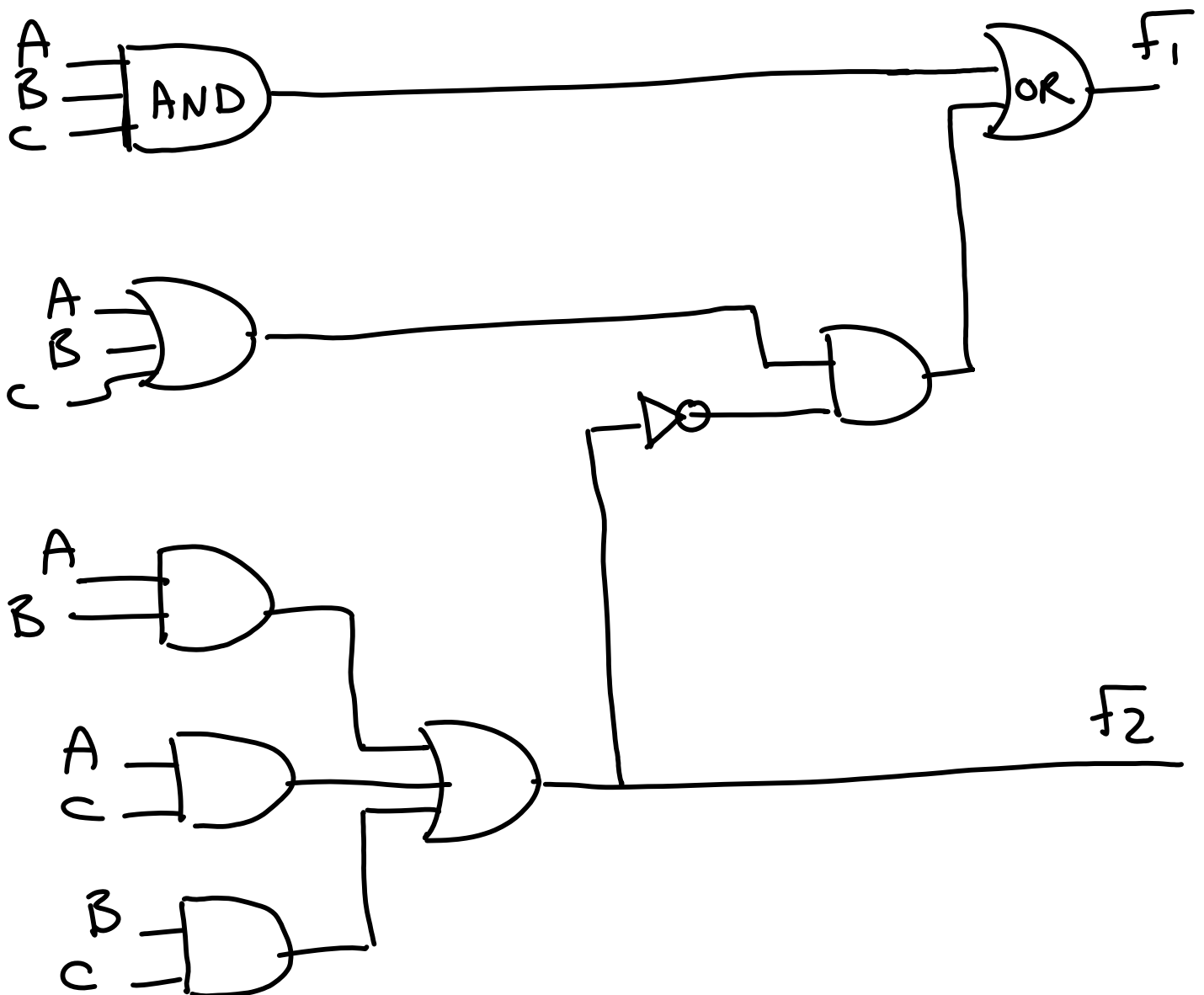


Medium Scale Integrated Circuit MSI

Ex

what are the output
function F_1, F_2 ?



$\textcircled{F_2}$

A \ BC	00	01	11	10
0			1	
1		1	1	1

$$F_2 = AC + AB + BC$$

A \ BC	00	01	11	10
0		1		1
1	1		1	

$$F_1 = A \oplus B \oplus C$$

Ex Design a logic circuit that convert a BCD digit into Excess-3

A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0				
1	0	1	1				
1	1	0	0				
1	1	0	1				
1	1	1	0				
1	1	1	1				

Do Not
Care

$$w = \sum (5, 6, 7, 8, 9)$$

$$x = \sum (1, 2, 3, 4, 9)$$

$$Y = \sum (0, 3, 4, 7, 8)$$

$$Z = \sum (0, 2, 4, 6, 8) \Rightarrow \text{by inspection} \\ Z = \overline{D}$$

CD \ AB	00	01	11	10
00				
01		1	1	1
11	X	X	X	X
10	1	1	X	X

$$\textcircled{W} = A + BD + BC$$

CD \ AB	00	01	11	10
00		1	1	1
01	1			
11	X	X	X	X
10		1	X	X

$$\textcircled{X} = B\overline{C}\overline{D} + \overline{B}D + \overline{B}C$$

CD \ AB	00	01	11	10
00	1		1	
01	1		1	
11	X	X	X	X
10	1		X	X

$$\textcircled{Y} = \overline{C}\overline{D} + CD$$

Prob

Sketch the logic diagram of the
Circuit above.

Ex


Design a logic circuit that can add two 1-bit number.


X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

⇒ you do not need to go to karnaugh

$$S = \bar{X}Y + X\bar{Y}$$

$$C = XY$$

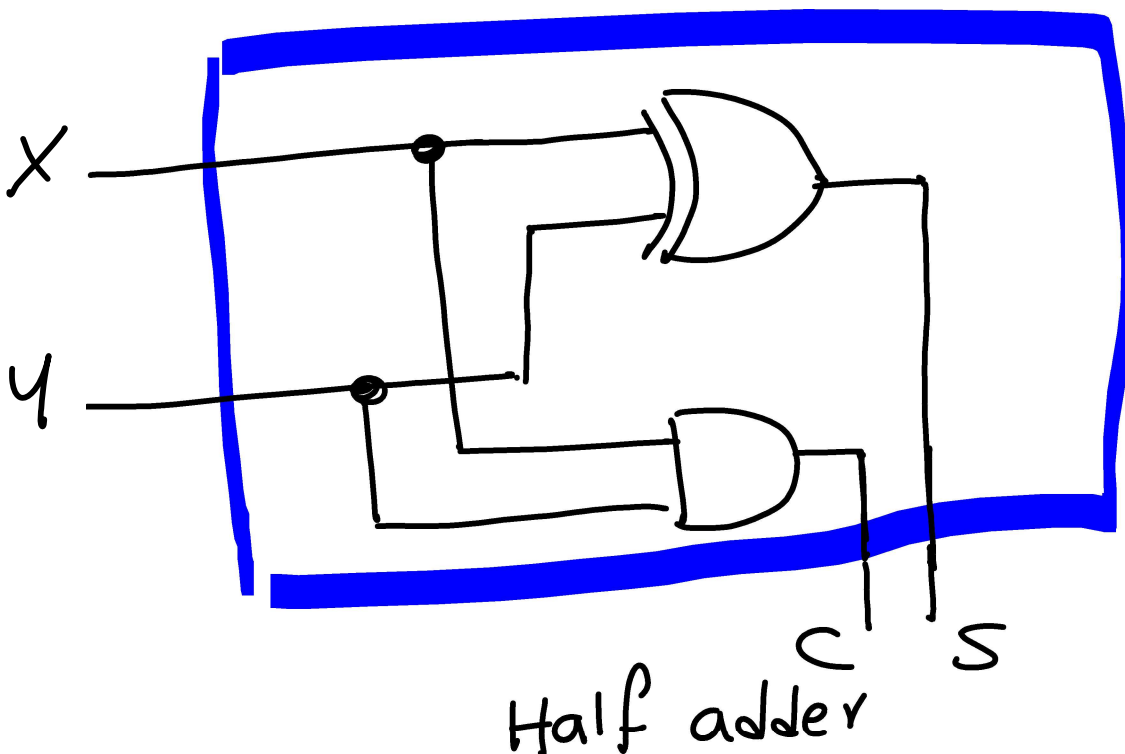

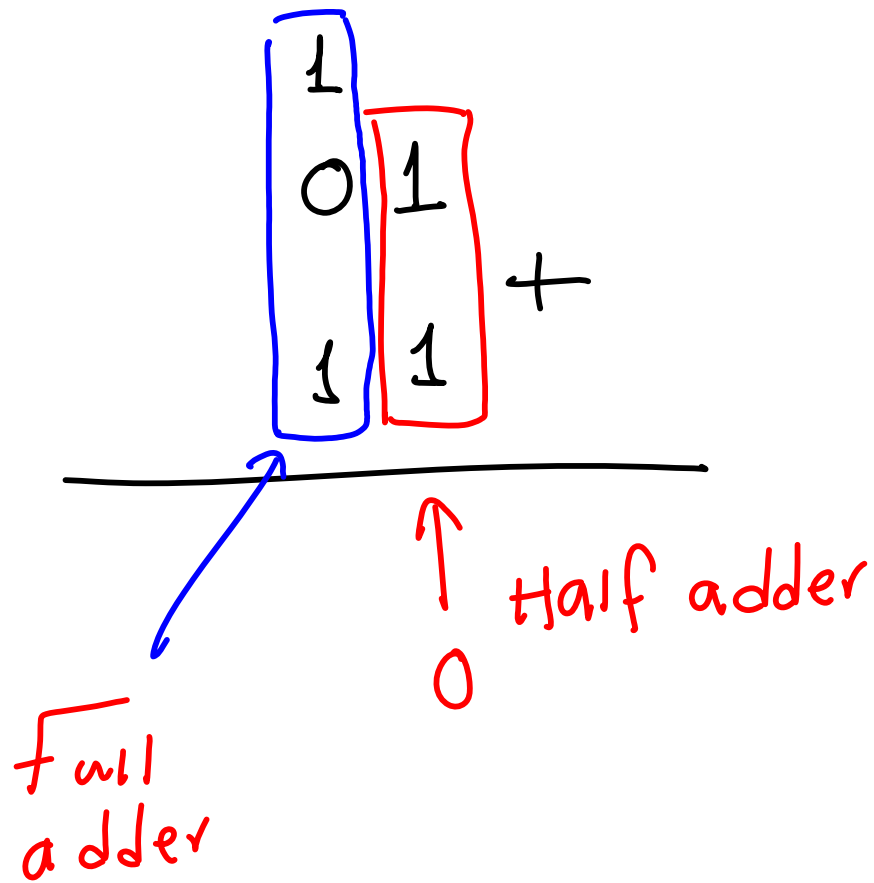

Ex

Design a digital logic circuit that can add two 1-bit number in addition to carry in

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$C = \sum (3, 5, 6, 7)$$


$$\Rightarrow S = \sum (1, 2, 4, 7)$$

$x \backslash yz$	00	01	11	10
0			1	
1		1	1	1

$$C = xy + xz + yz$$

$x \backslash yz$	00	01	11	10
0		1		1
1	1		1	


$$S = x \oplus y \oplus z$$

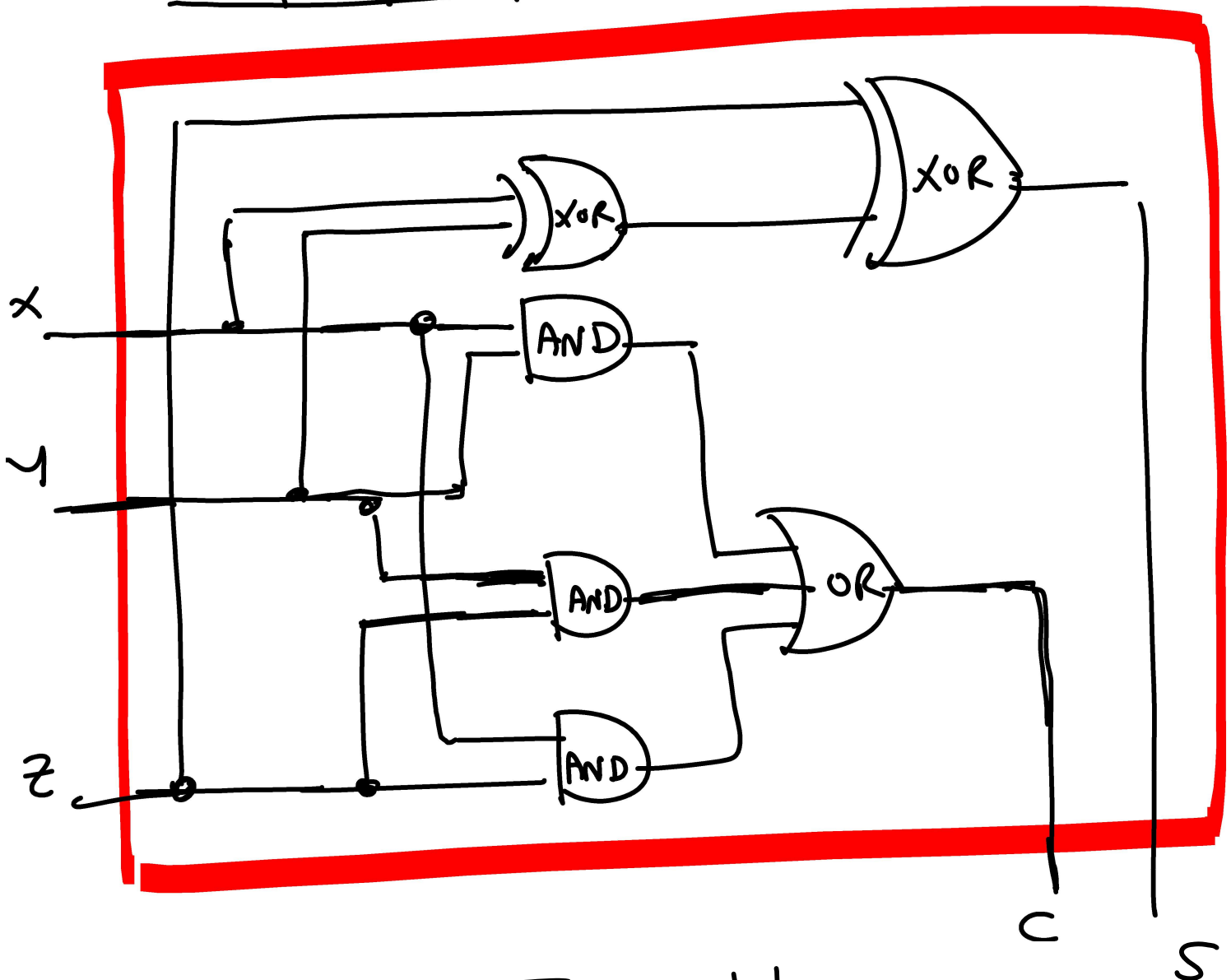


full adder

Note
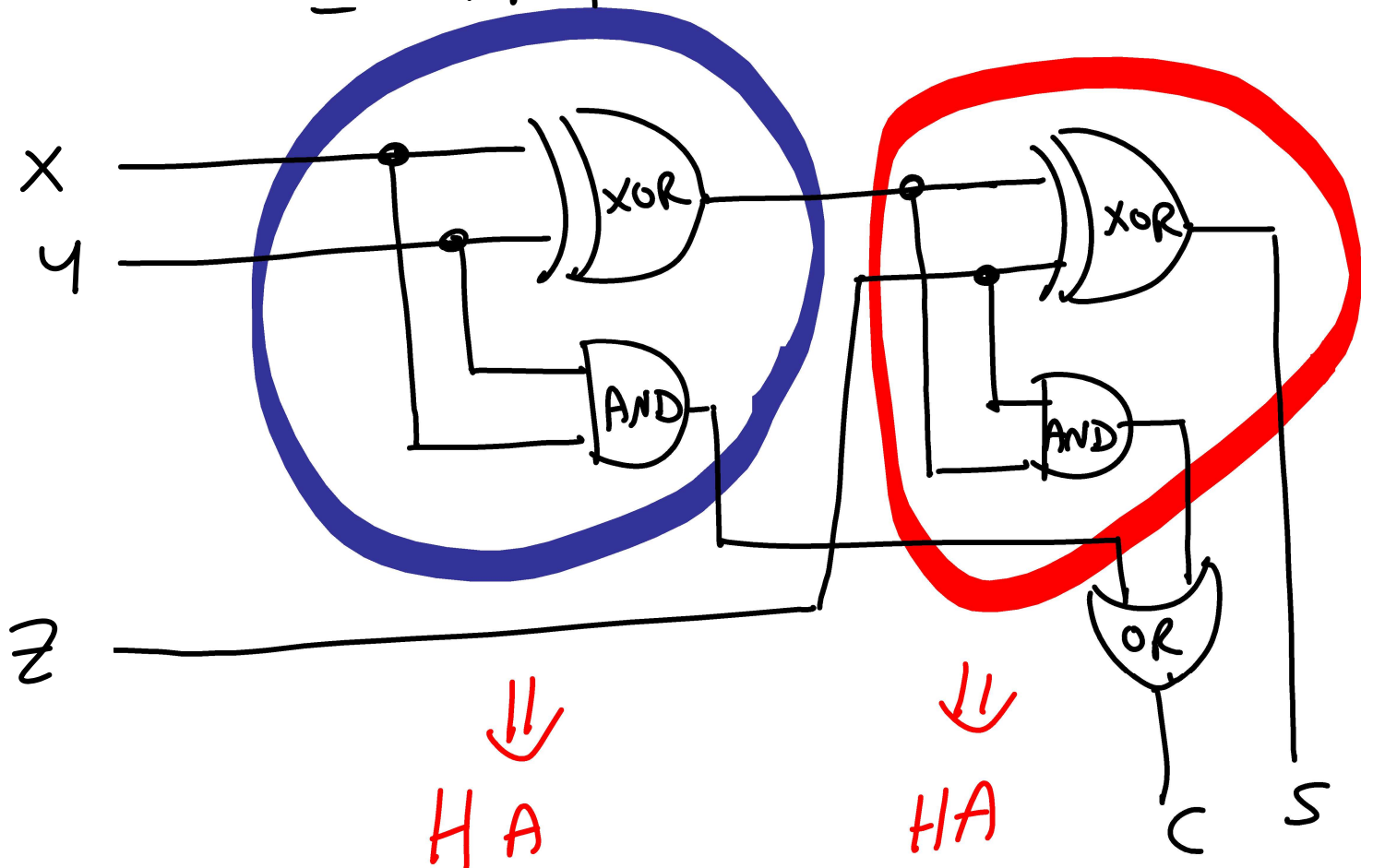
$$\begin{aligned} \text{C} &= xy + xz + yz \\ &= xy + z(x + y) \\ &= xy + z(x(y + \bar{y}) + (x + \bar{x})y) \\ &= xy + z(xy + x\bar{y} + x\bar{y} + \bar{x}y) \\ &= xy + z(xy + x \oplus y) \\ &= xy + z(x \oplus y) \end{aligned}$$



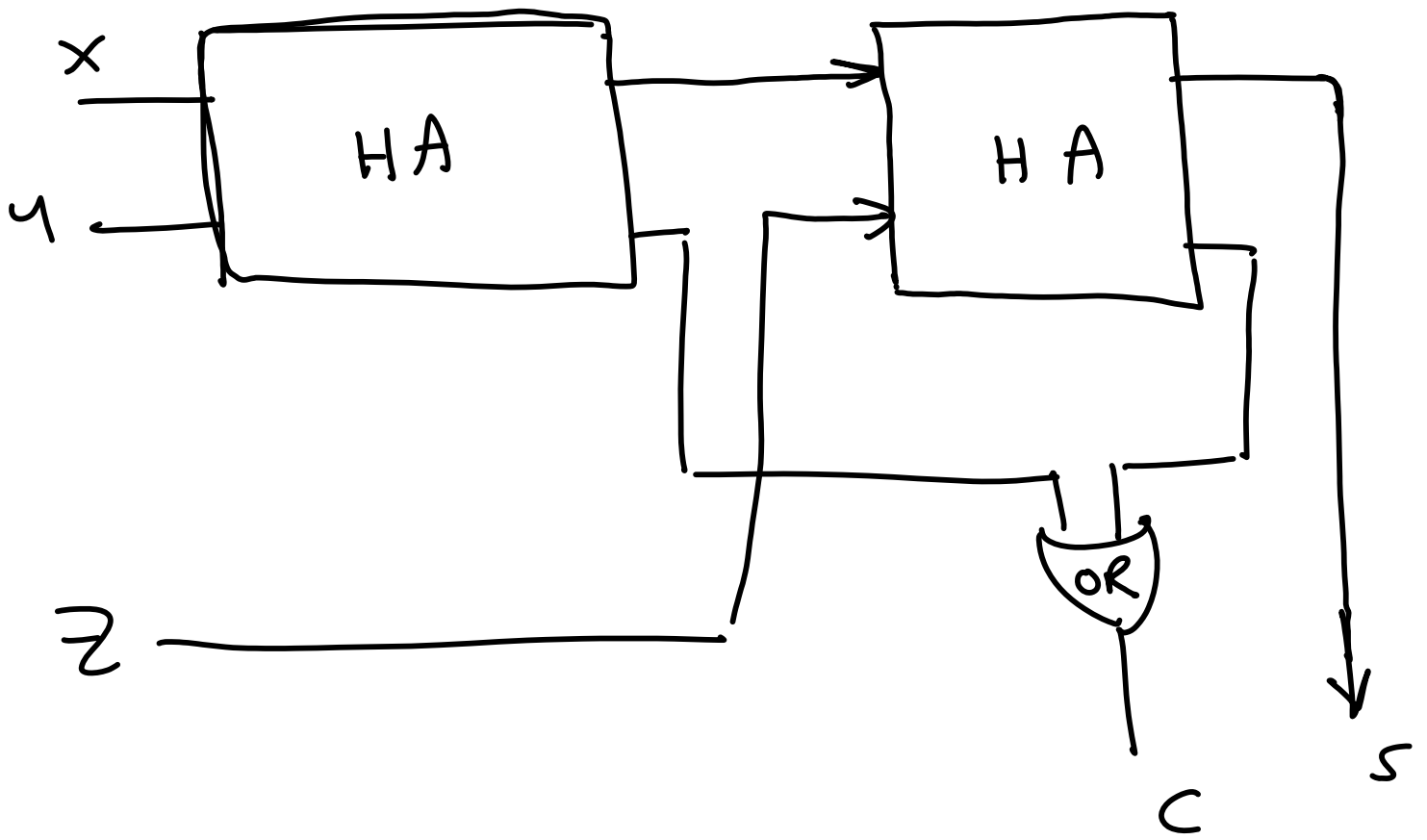

Ex

Design a logic circuit that can add two 2-bit number

A_1	A_0	B_1	B_0	C_2	C_1	C_0
						

why 3 bits
in output

Ex

Design a logic circuit that can add two 4-bit number

A_3	A_2	A_1	A_0	B_3	B_2	B_1	B_0	C_4	C_3	C_2	C_1	C_0
-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------



+1 carry

9 inputs

5 output

9
2 entries


Hierarchical Design

- We divide our design into smaller functional block
- Connect functional units to produce the big functionality
- How can we build an n -bit adder from full-adders?
 - one adder for each bit (n total)
 - Connect carry to next adder's input
 - Sequence of sums and final carry are results

Note

$$\begin{array}{cccc} 1 & 1 & 1 & 0 \\ \hline 1 & 1 & 0 & 1 \\ 0 & 0 & 1 & 1 \end{array} +$$

1 0 0 0 0

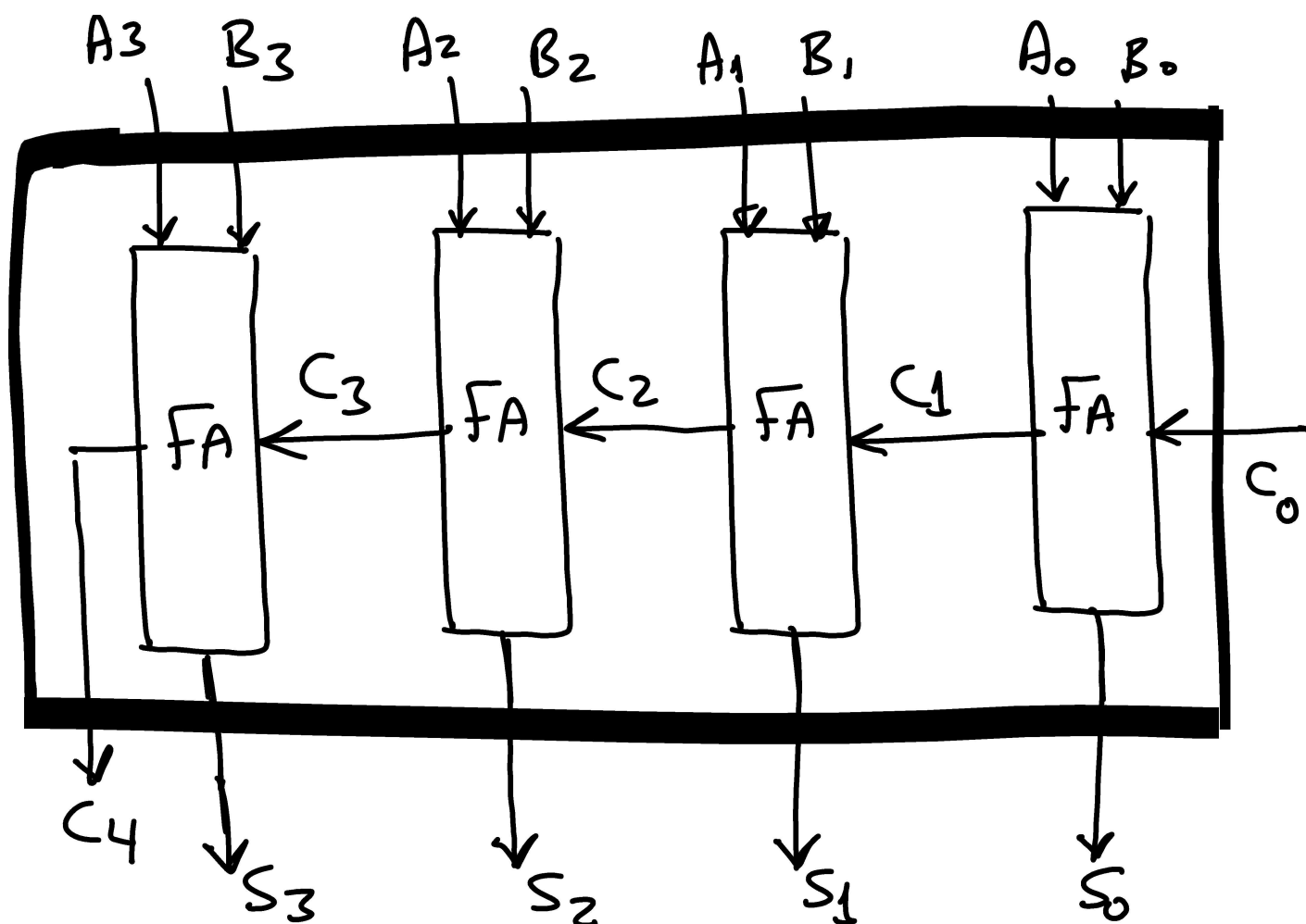

Note


- the addition of two binary numbers in parallel implies that all the bits of the augend and addend are available for computation at the same time
- As in any combinational circuit, the signal must propagate through the gates before the correct output sum is available in the output terminals
- the total propagation time is equal to the propagation delay of a typical gate times the number of gate levels in the circuit
- the longest propagation delay time in an adder is the time it takes the carry to propagate through the full-adders

Report


- What is propagation delay time?
- How can we know AND gate propagation time?
- How can we speed up addition?
 - ↳ Note carry lookahead
- Carry lookahead Generator
- Carry lookahead adder

Info Note

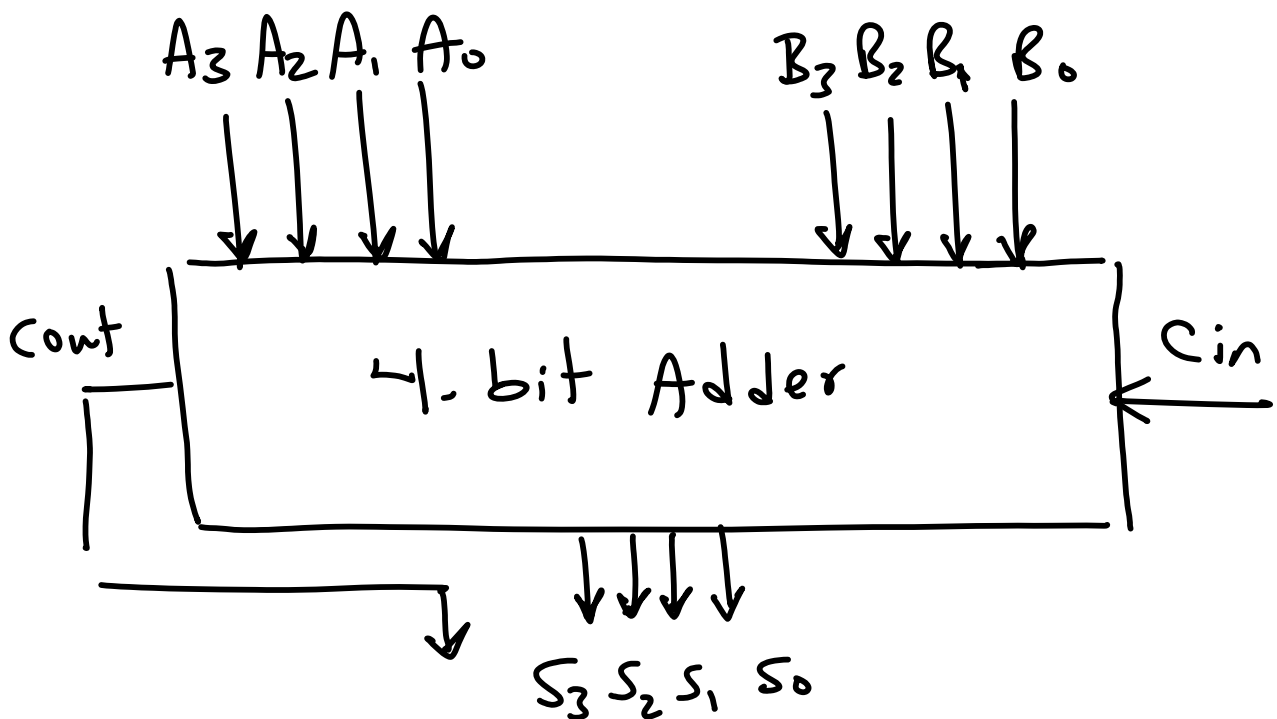
- Addition is performed by processors on two numbers at a time, called operands
- The source operand is a number that is to be added to an existing number called destination operand, which is held in an ALU register, such as the accumulator
- the sum of the two numbers is then stored back in the accumulator



Practical Session

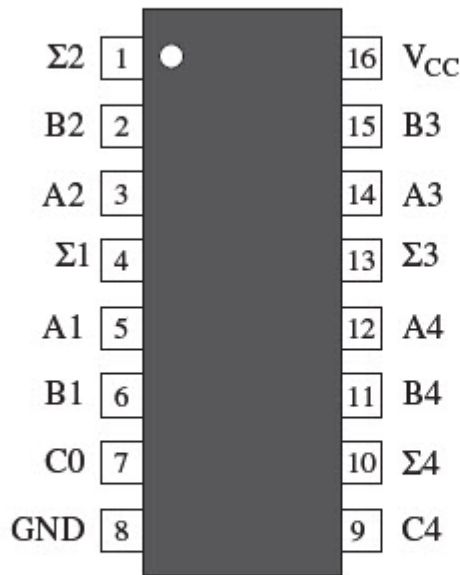

(a) Pin diagram

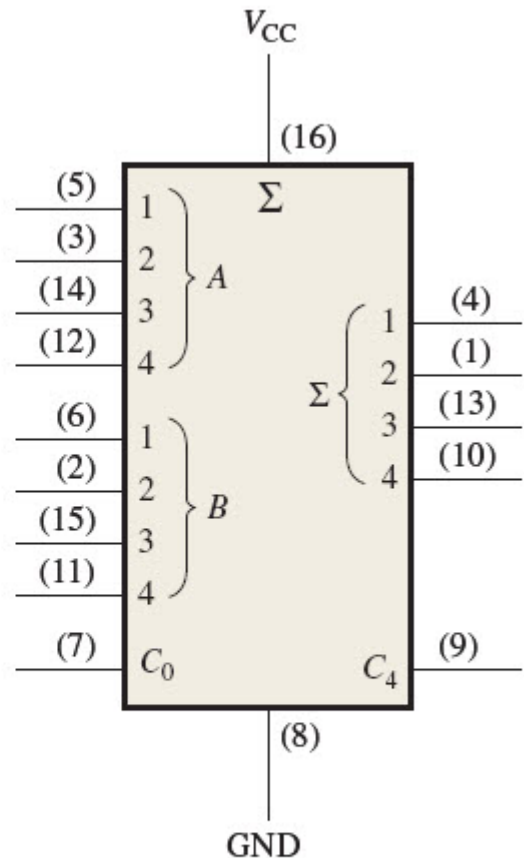

(b) Logic symbol

The 74HC283/74LS283 4-bit parallel adder.

Report


- MultiSim
- proteus
- Printed Circuit board
- Goto electronic shop

Note

the 4-bit parallel adder can be expanded to handle more bits by cascading

Report

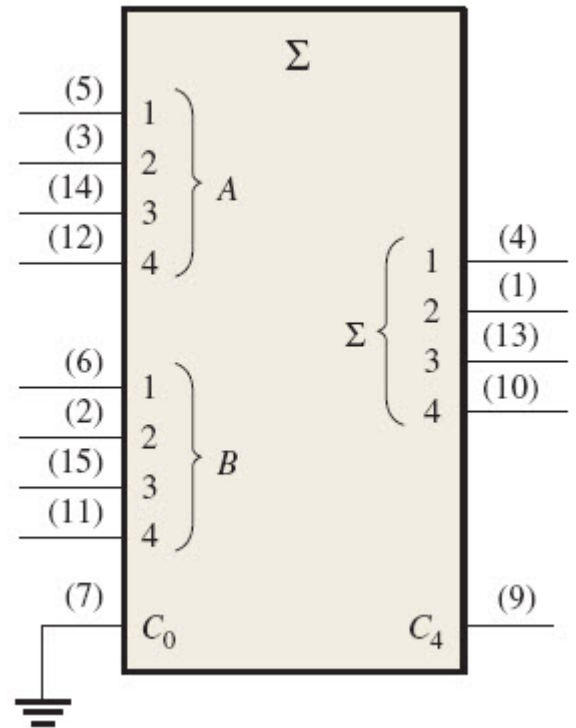show how two 74HC283 can be connected to form an 8-bit parallel adder




Report

use 74HC283 adders to implement a 12-bit parallel adder.

Voting System

An example of full-adder and parallel adder application is a simple voting system that can be used to simultaneously provide the number of "yes" votes and the number of "no" votes •

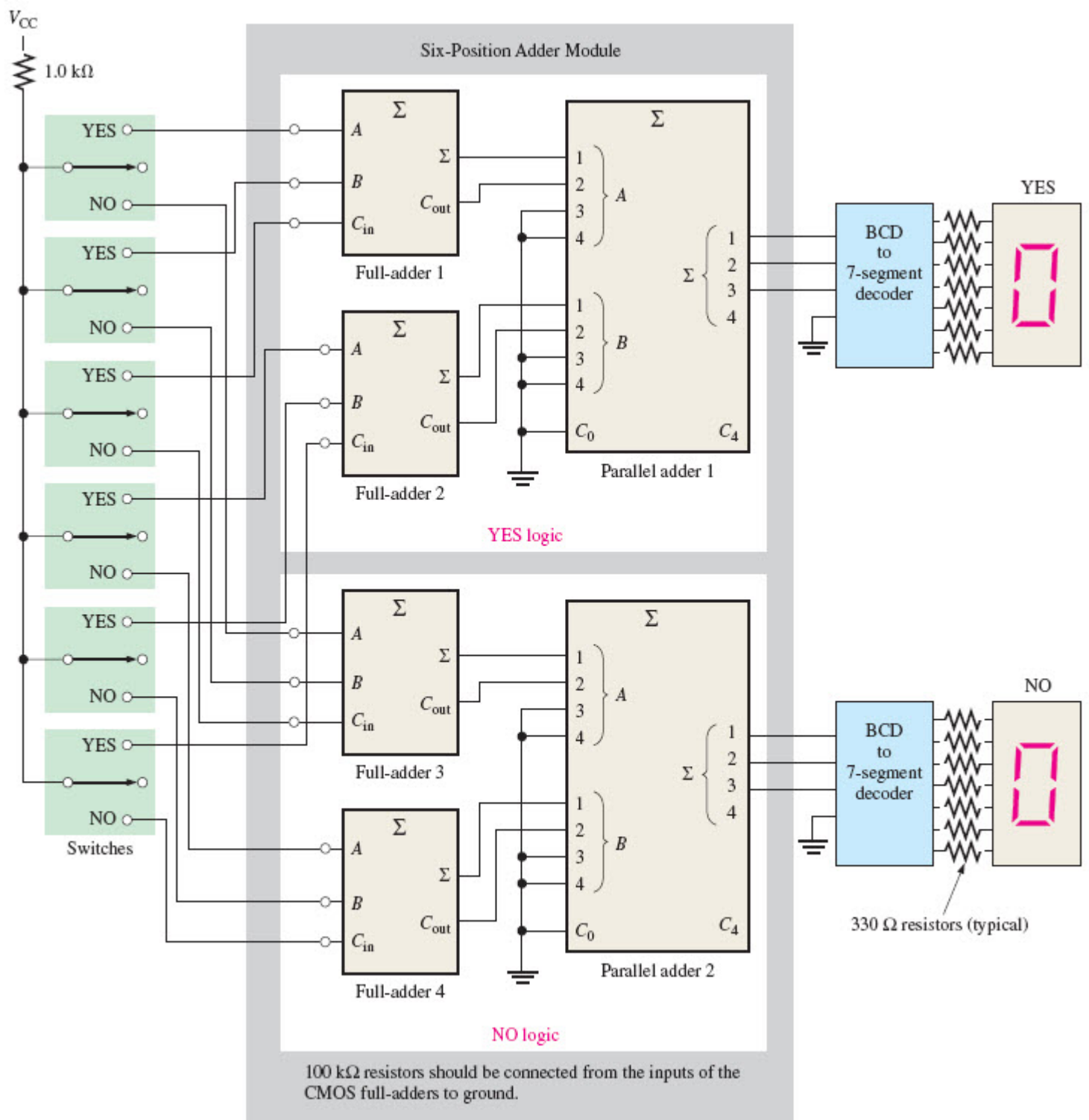this type of system can be used where a group of people are assembled and there is a need for immediately determining opinions (for or against), making decisions, or voting on certain issues or other matters



Next lecture ToC

- Subtractors
- Multipliers
- Comparators

using 4-bit
←
excess-3
Converter

