

Ex


Design a digital circuit that can select between two 1-bit number I_0, I_1 . the output should be $Y = I_0$ when $S = 0$, and $Y = I_1$ when $S = 1$

$$Y = \begin{cases} I_0 & S = 0 \\ I_1 & S = 1 \end{cases}$$


S	I_0	I_1	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$I_0 I_1$		S			
		00	01	11	10
0	0			1	1
1	0		1	1	

$$Y = \overline{S} I_0 + S I_1$$

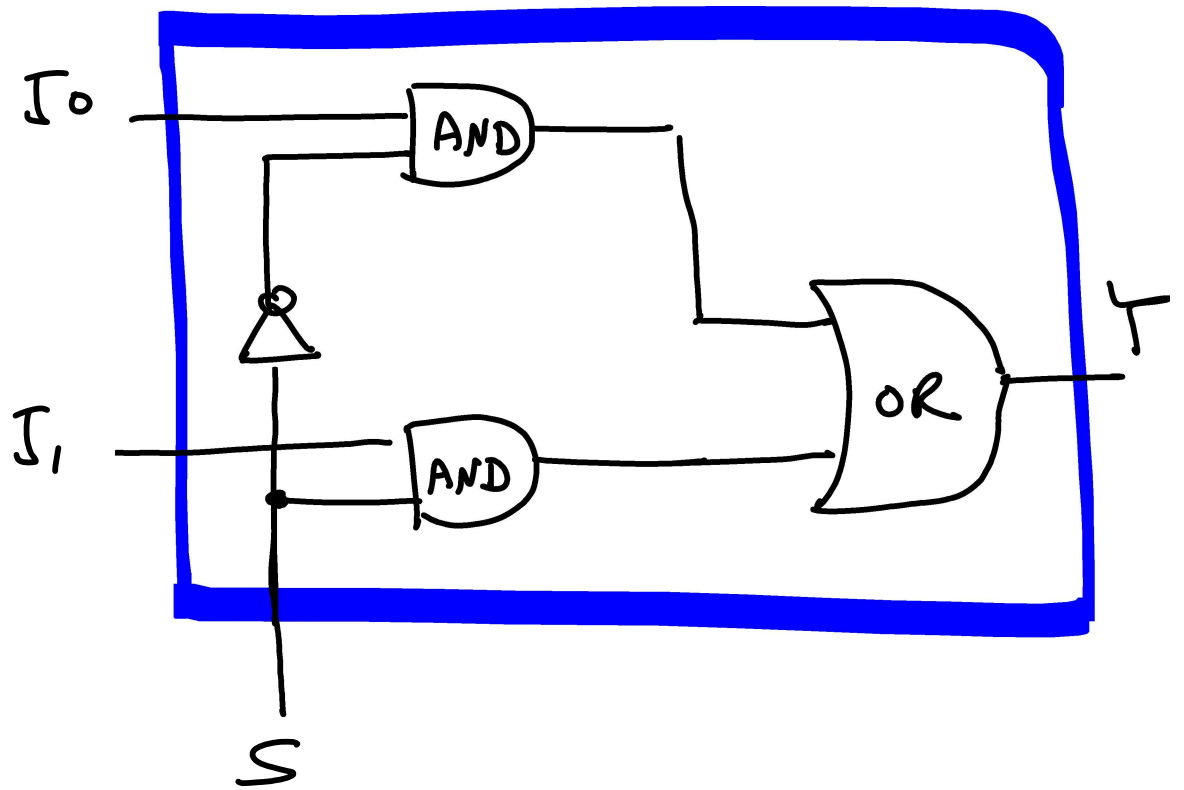

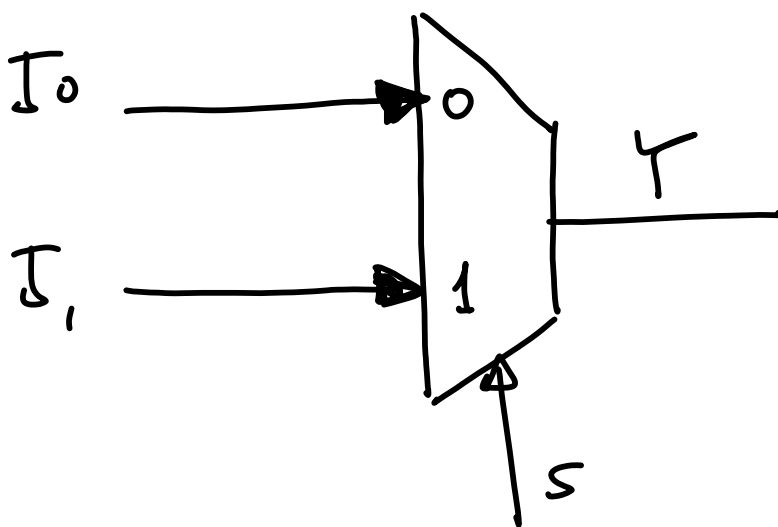this circuit is called Multiplexer
 2×1 Multiplexer



2×1 Mux

A multiplexer (MUX) is a device that allows digital information from several sources to be routed onto a single line for transmission over that line to a common destination


Inputs : 2^n input lines
 n selection bits

Output : 1 output line

Ex 2×1 MUX

we can use
function table

S	Y
0	I_0
1	I_1

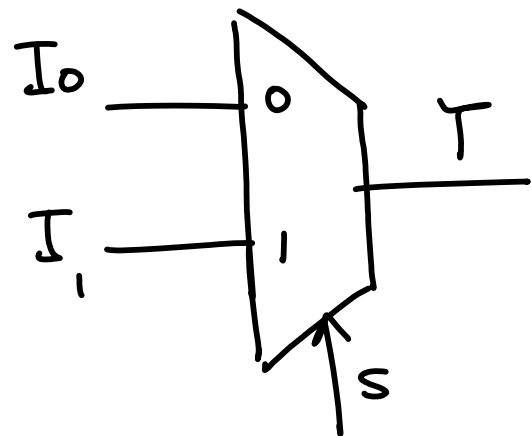


$\rightarrow Y = \bar{S}I_0 + SI_1$

Ex


4x1 Mux

S_1, S_0		Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3
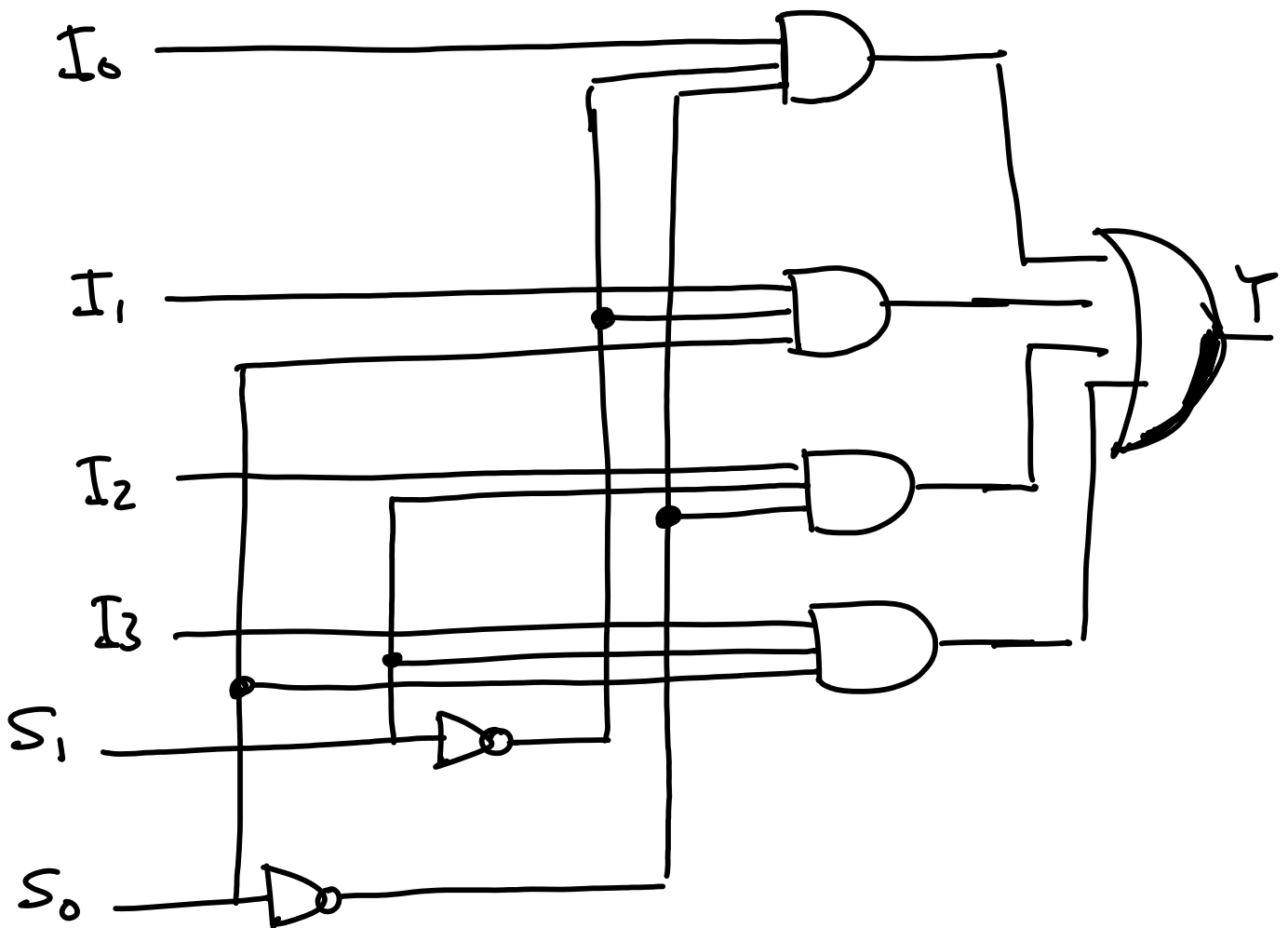
$$\Rightarrow Y = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$$



4x1 Mux

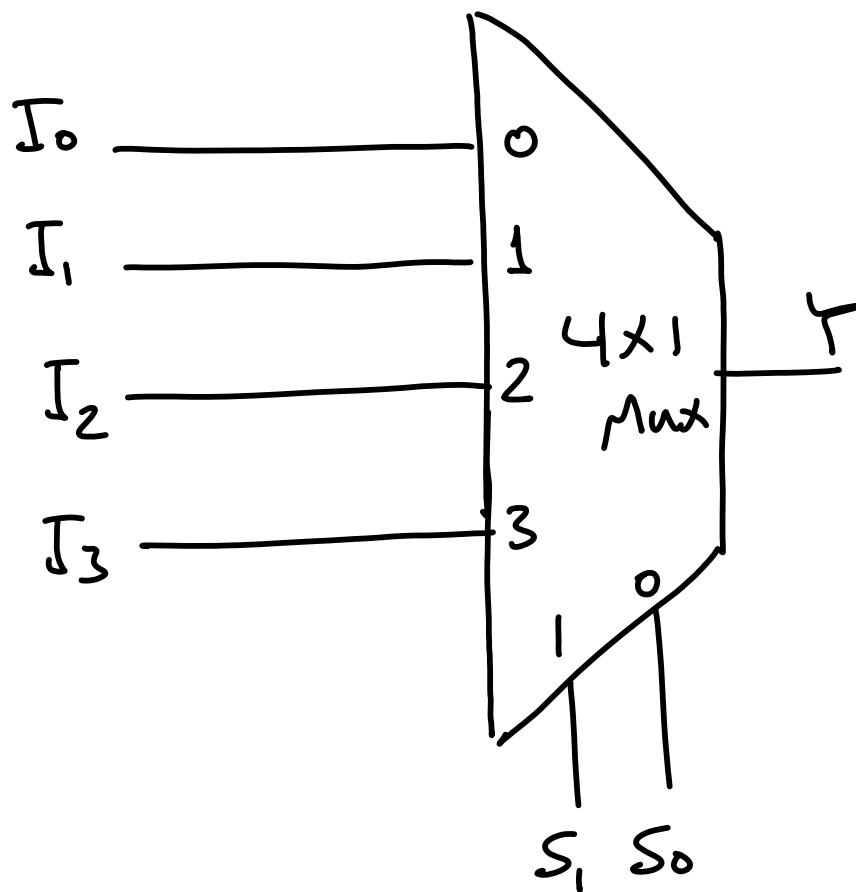

InfoNote

A bus is a multiple conductor pathway along which electrical signals are sent from one part of a computer to another.

In a computer networks, a shared bus is one that is connected to all the microprocessors in the system in order to exchange data.

A shared bus may contain memory and input/output devices that can be accessed by all the microprocessors in the system.

Access to the shared bus is controlled by a bus arbiter that allows only one microprocessor at a time to use the system's shared bus.


Note

Multiplexer $\equiv$ Data Selector

74HC153 $\Rightarrow$ dual four-input data
Selector / multiplexer


- the inputs to one of the multiplexers are $1I_0$ through $1I_3$
- the inputs to the second multiplexer are $2I_0$ through $2I_3$

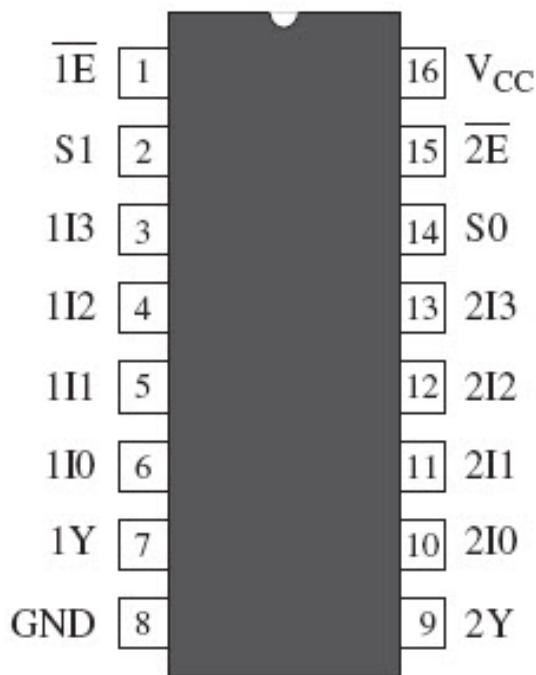- the data select inputs are S_0 and S_1 and the active-low enable inputs are $1\overline{E}$ and $2\overline{E}$ — each of the multiplexers has an active-low enable input



The 74HC153 dual four-input data selector/multiplexer.

74HC151 : 8X1
Mux

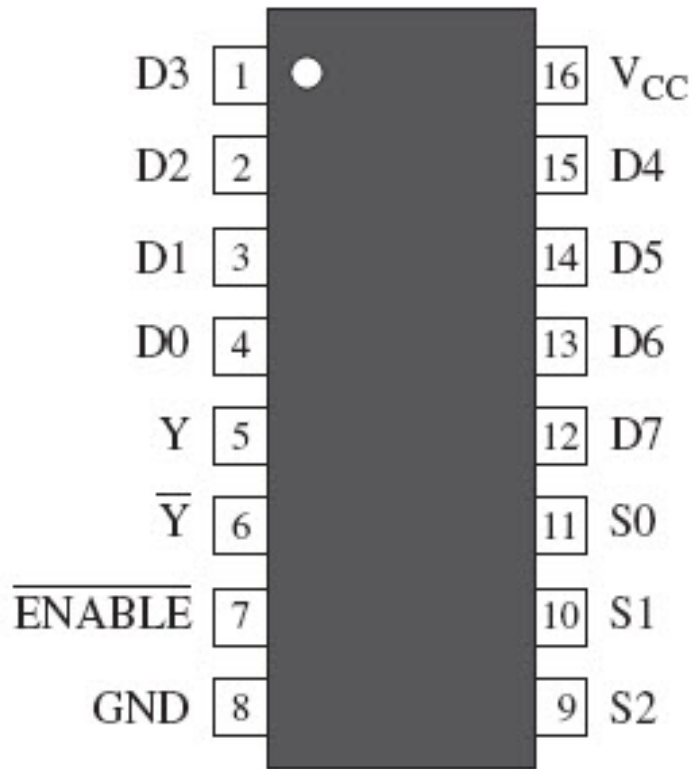


The 74HC151 eight-input data selector/multiplexer.

Notice that the data output and its complement are both available

Report :

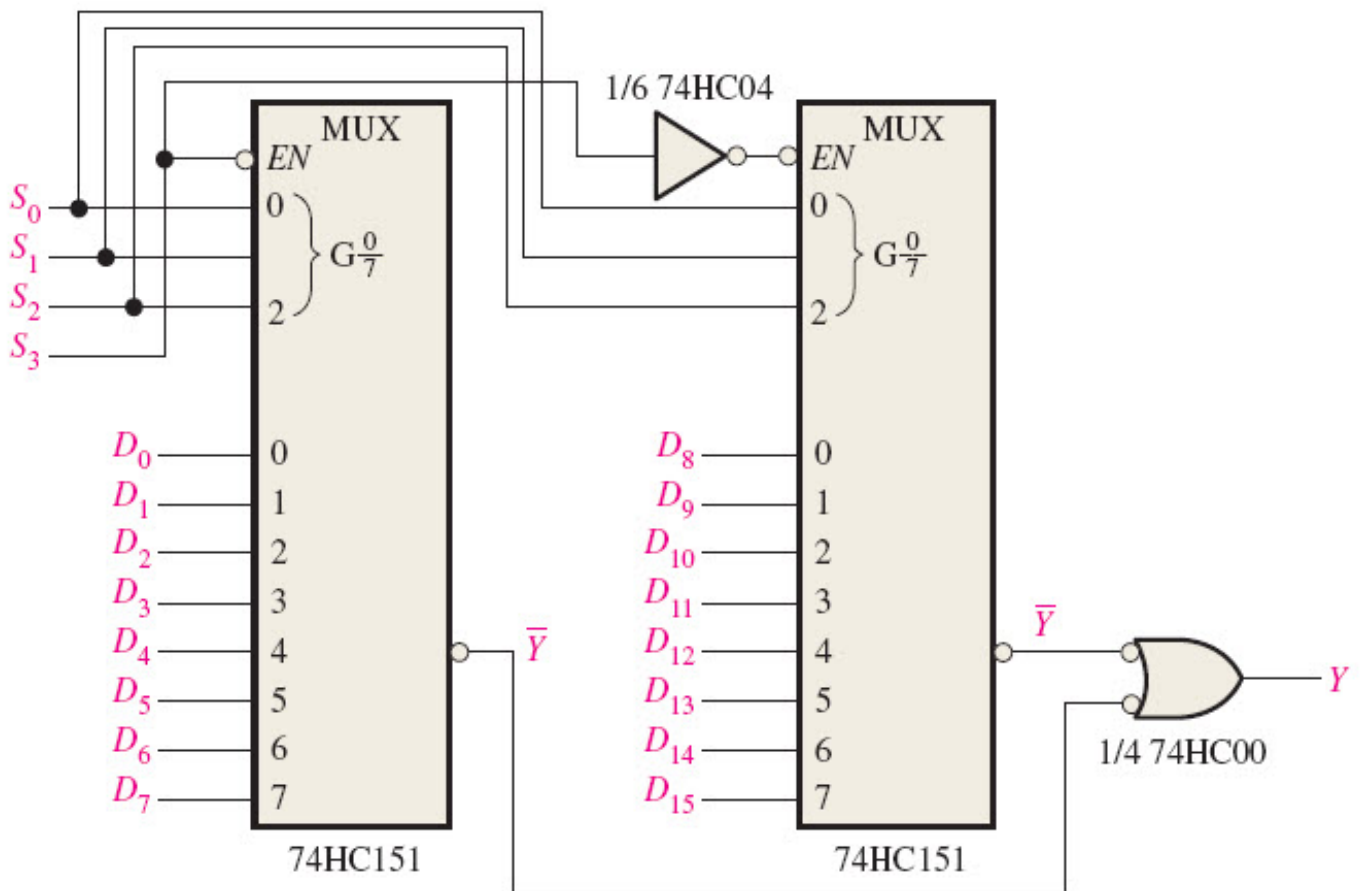use 74HC151s and any other logic necessary to multiplex 16 data lines onto a single data-output line.




A 16-input multiplexer.

Prob :

Determine the codes on the select inputs required to select each of the following data inputs: D_0 , D_4 , D_8 , D_{13}

Ex choose one of two 4-bit numbers

Sol Quadrable 2x1 Mux

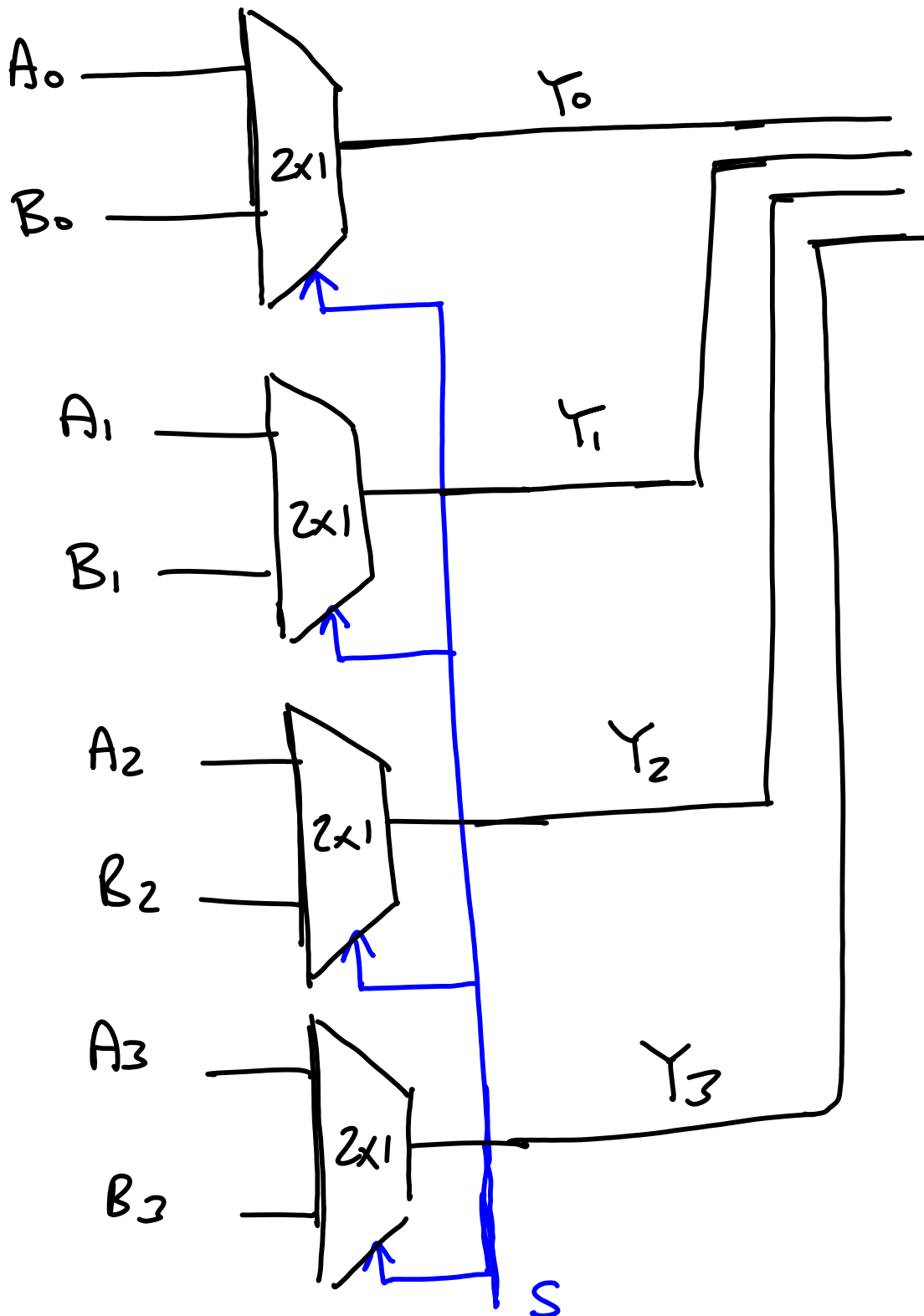


Function implementation with Mux

- function with n variables has 2^n truth table entries
 - wire up 1 and 0 to each input of 2^{n-1} to 1 line mux
- Can be done more efficiently
 - 2^{n-1} to 1 mux sufficient
- Idea
 - wire up $n-1$ variables to selection bits
 - function might depend on n th variable
 - use for 2^{n-1} inputs

Ex implement the Boolean function F represented in the truth table below


x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

What is the
relation between
 F and z

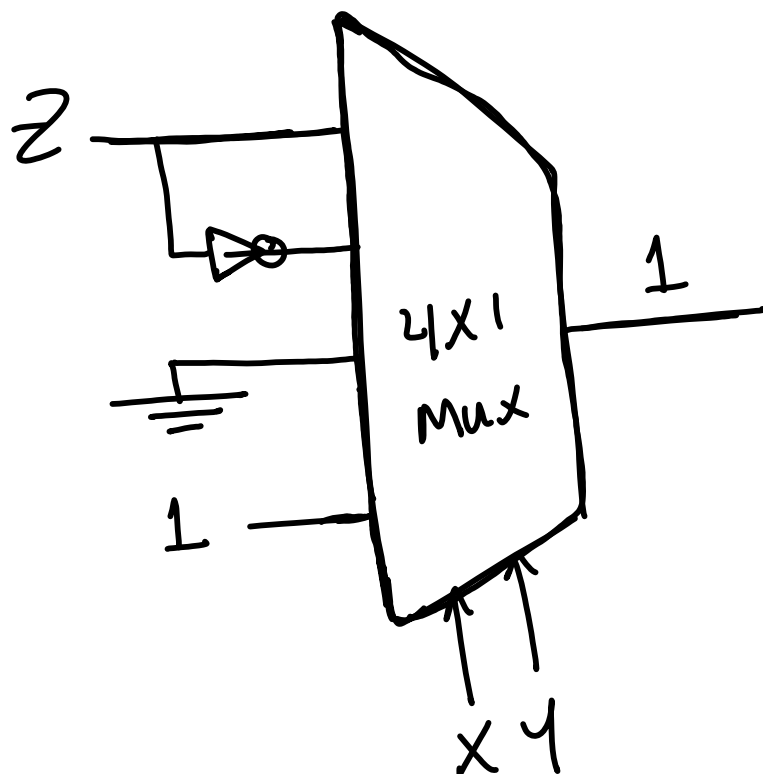


Ex

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

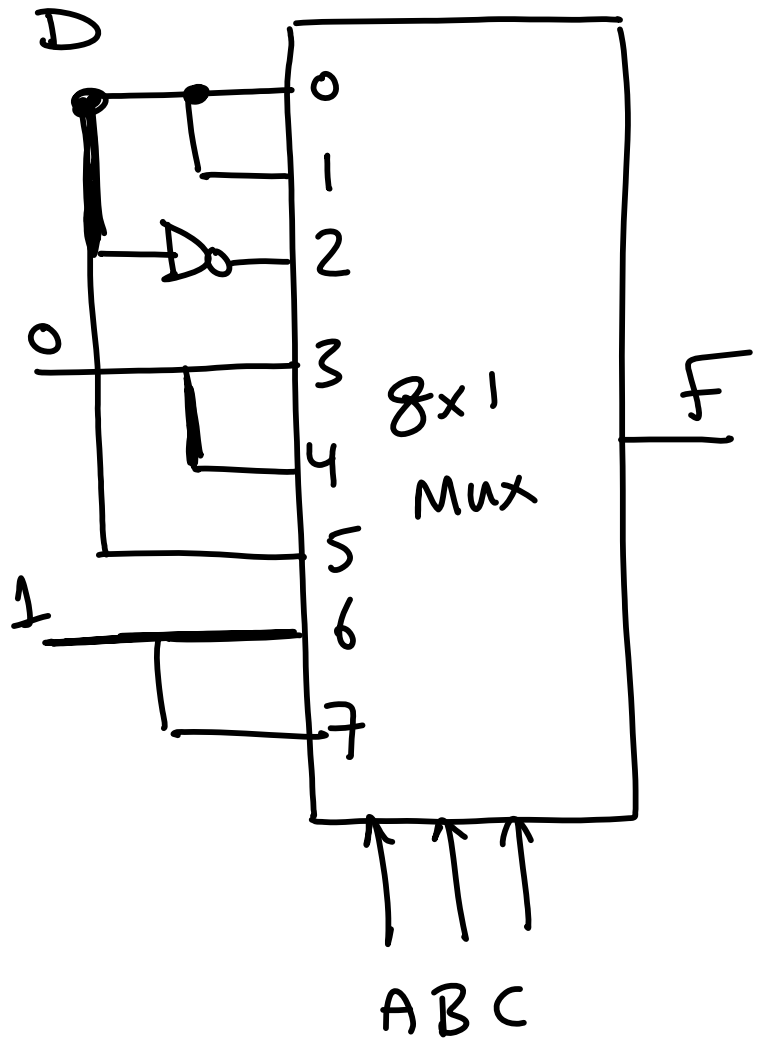


Three - state Gate

Did you see this circuit before?

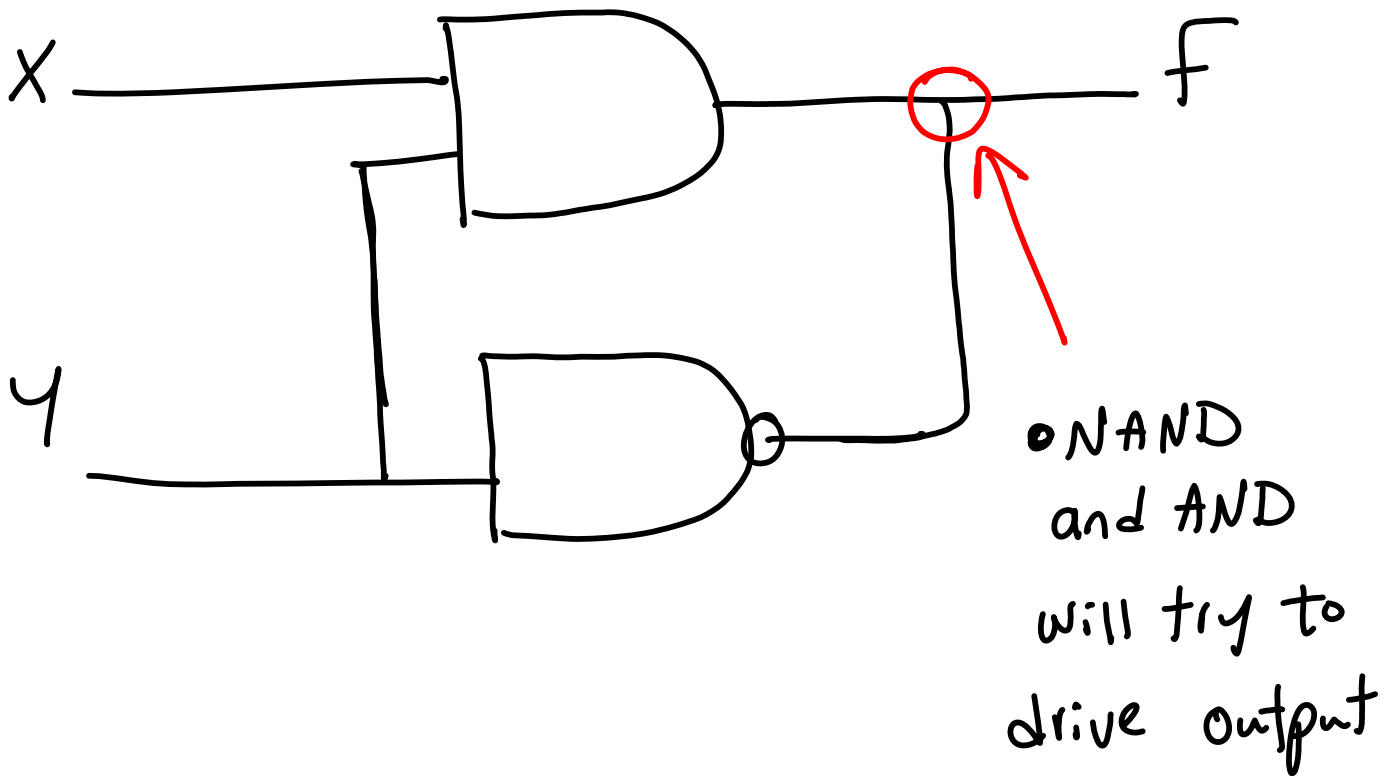

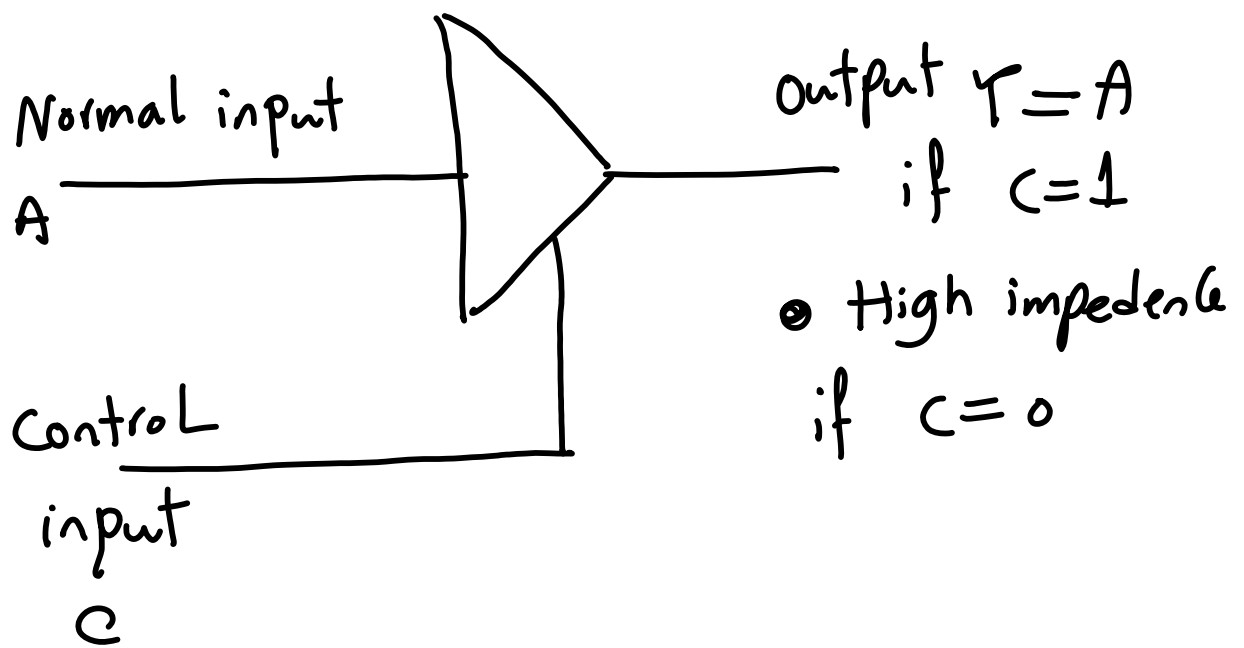
- Sometimes necessary to disconnect a gate
- three state
 - 0 or 1 Boolean value
 - High impedance



- High impedance acts as if gate is disconnected
- A different type of logic gate
 - Instead of two states (0, 1), it exhibits three states (0, 1, Z)
- Z is called high impedance
- when in Z-state, the circuit behaves like an open circuit (the output behaves like an open circuit)
(the output appears to be disconnected,

and the circuit has no logic significance)

Multiplexer with three-State gate

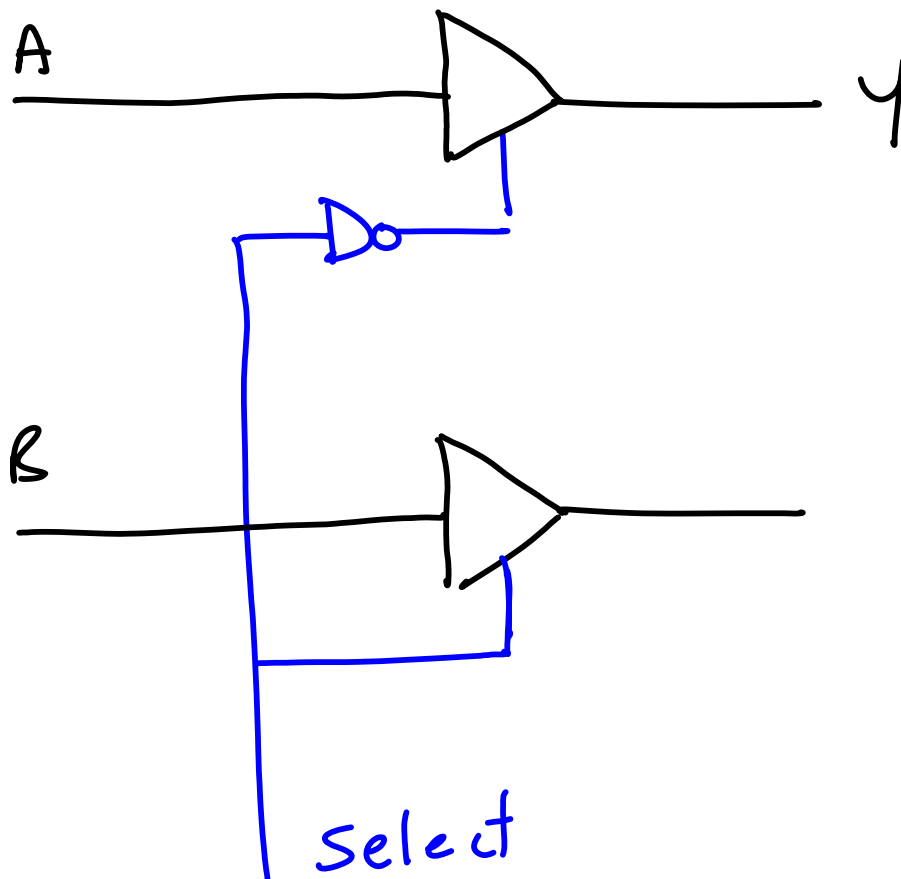

2x1 mux

