

System model

Electric circuit

- electric circuits are frequently used in control systems largely because of the ease of manipulation and processing of electric signals.
- Although controllers are increasingly implemented with digital logic, many functions are still performed with analog circuit

- ① analog circuits are faster than digital, and for very simple controllers, an analog circuit would be less expensive than a digital implementation
- ② Furthermore, the power amplifier for electromechanical control and the anti-alias pre-filters for digital control must be analog circuit


Kirchhoff's laws

① Kirchhoff's Current law KCL
the algebraic sum of currents leaving a junction or node equals the algebraic sum of currents entering that node

② Kirchhoff's voltage law KVL
the algebraic sum of all voltages taken around a closed path in a circuit is zero


i.e. ① $I_{in} = I_{out}$

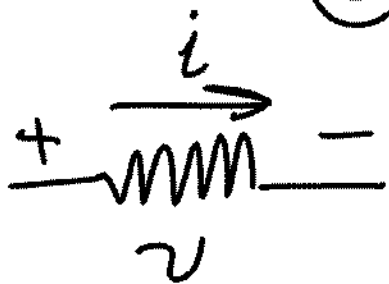② $\sum \text{voltage sources} = \sum \text{voltage drops}$




$$v(t) = i(t) \times R$$

$$V(\omega) = I(\omega) R$$

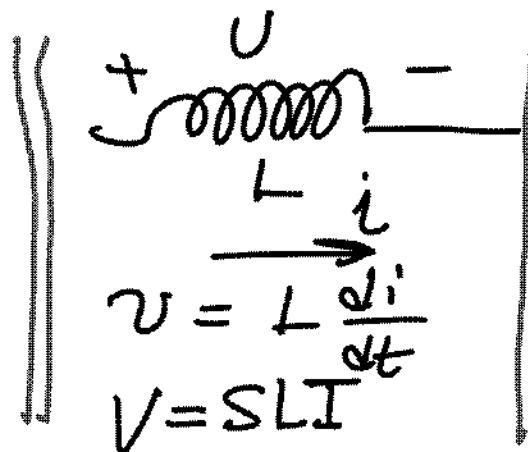

$$v = L \frac{di}{dt}$$


$$V = SLI$$

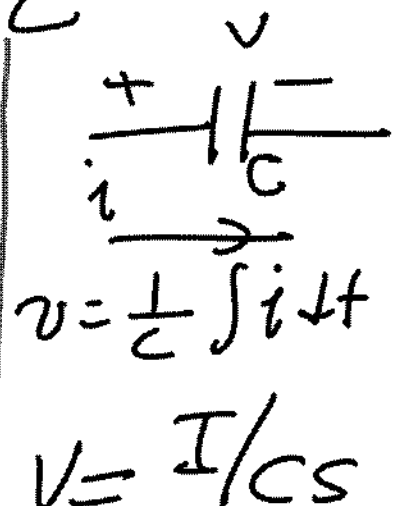

$$v = \frac{1}{C} \int i dt$$

$$V = I / C\omega$$

RLC Circuit

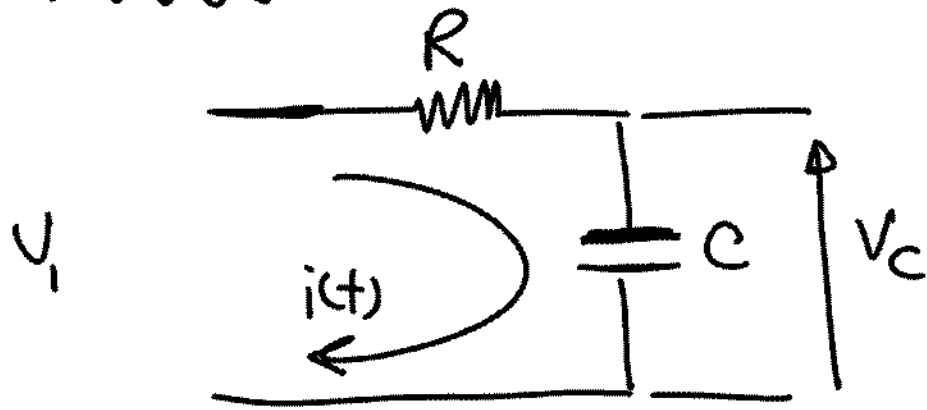

$$V_1(t) = i(t)R + \frac{1}{C} \int i(t) dt$$

↓ taking laplace

$$V_1(s) = I(s)R + \frac{I(s)}{Cs}$$

$$\Downarrow V_1 = IR + \frac{I}{Cs} = I\left(R + \frac{1}{Cs}\right) \rightarrow (1)$$

$$V_C(t) = \frac{1}{C} \int i(t) dt$$

$$\Downarrow V_C = \frac{I}{Cs} \rightarrow (2)$$


divide (2) by (1)

$$\text{so } \frac{V_C}{V_1} = \frac{1/CS}{R + 1/CS}$$

$$\frac{V_C}{V_1} = \frac{1}{1 + RCs}$$

mathematically $\Rightarrow$ analytically

$$\text{so } \frac{V_C}{V_1} = \frac{1/RC}{s + 1/RC}$$

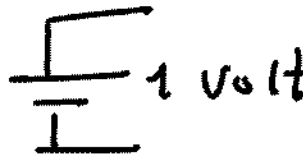Assume $V_1(t) = u(t)$  1 volt

$$V_1(t) = u(t) \Rightarrow V_1 = 1/s$$

$$V_C = \frac{1}{RC} * \frac{1}{s(s + 1/RC)}$$

$$\text{so } V_C = \frac{1}{RC} \left(\frac{RC}{s} - \frac{RC}{s + 1/RC} \right)$$


$$V_c = \frac{1}{s} - \frac{1}{s + 1/RC}$$

↓

$$V_c(t) = 1 - e^{-\frac{1}{RC}t}$$

Assume $R=1$, $C=0.0001$

so $V_c(t) = 1 - e^{-10000t}$ like this

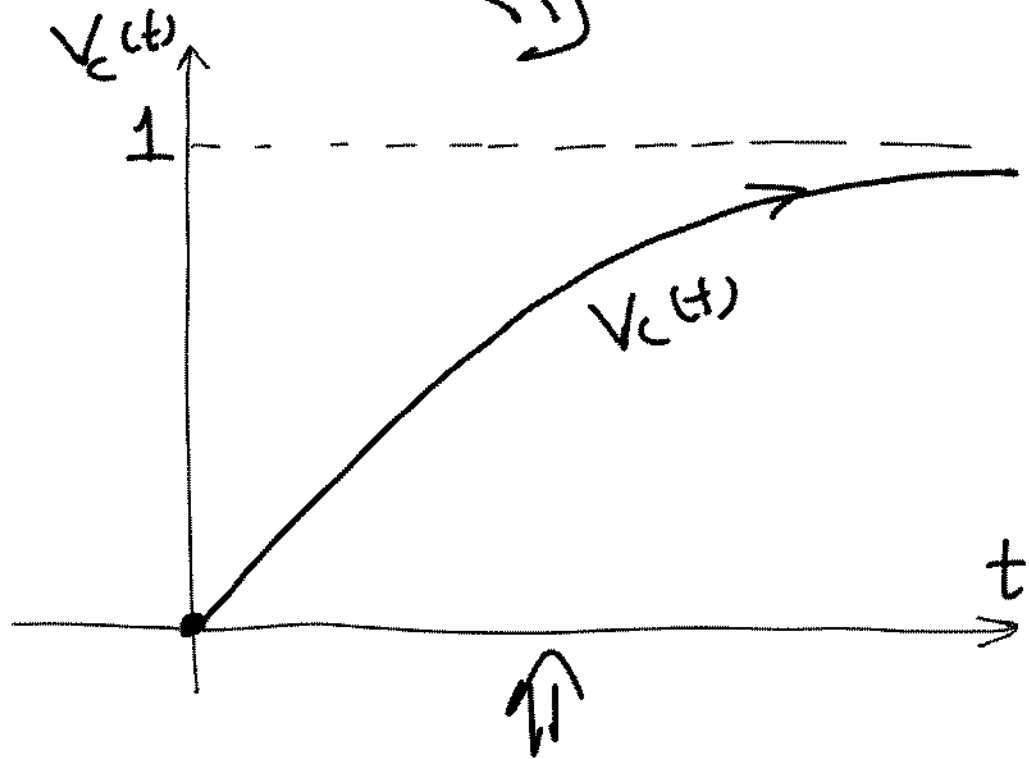

charging capacitor

② by MATLAB $\Rightarrow$.m file

$$\frac{V_c}{V_i} = \frac{1}{1 + RCs}$$

Assume

$\hookrightarrow$

$V_i = u(t) \Rightarrow$ unit step

$R = 1 \Omega$

$C = 0.0001$

$R = 1;$

$C = 0.0001;$

$num = 1;$


$den = [R \times C \quad 1];$

$sys = tf(num, den);$

$t = 0 : 0.001 : 0.01;$

$V_c = step(sys, t);$

$plot(t, V_c)$

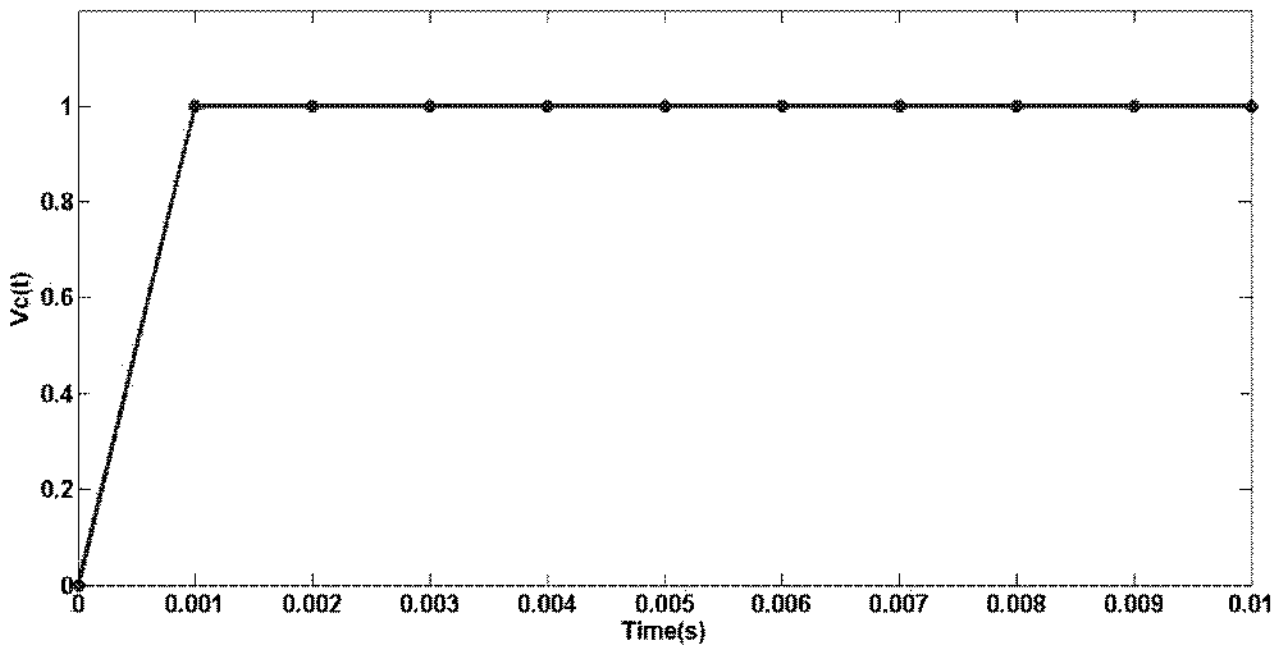

③ MATLAB // SIMULINK



$$\frac{V_c}{V_i} = \frac{1}{1 + RCs}$$


⇓ taking inverse Laplace

$$V_c + RC V_c' = V_i$$



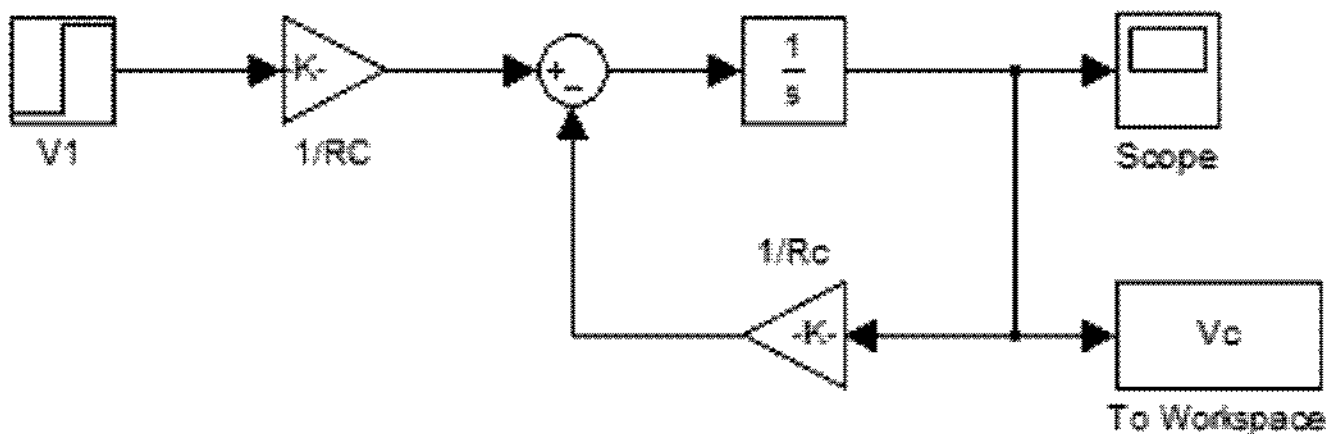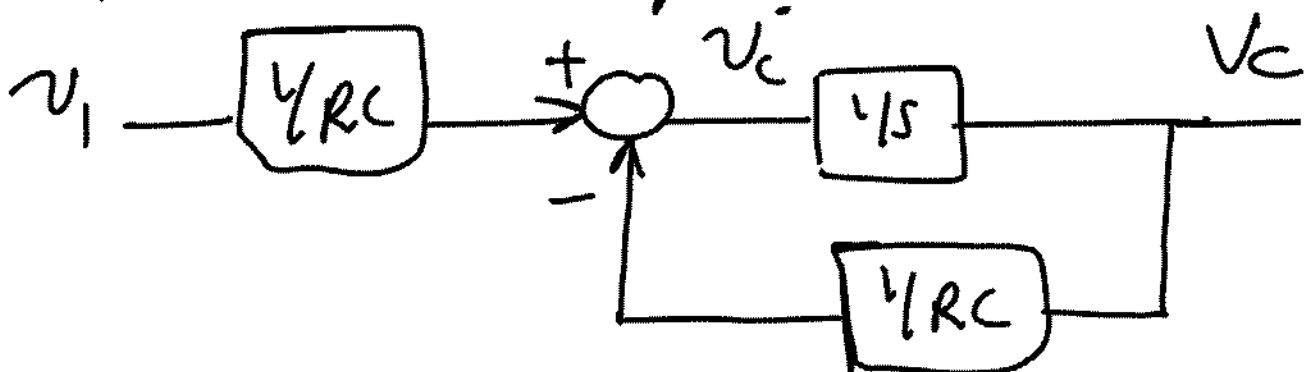
$$\frac{1}{RC} V_c + V_c' = \frac{1}{RC} V_i$$



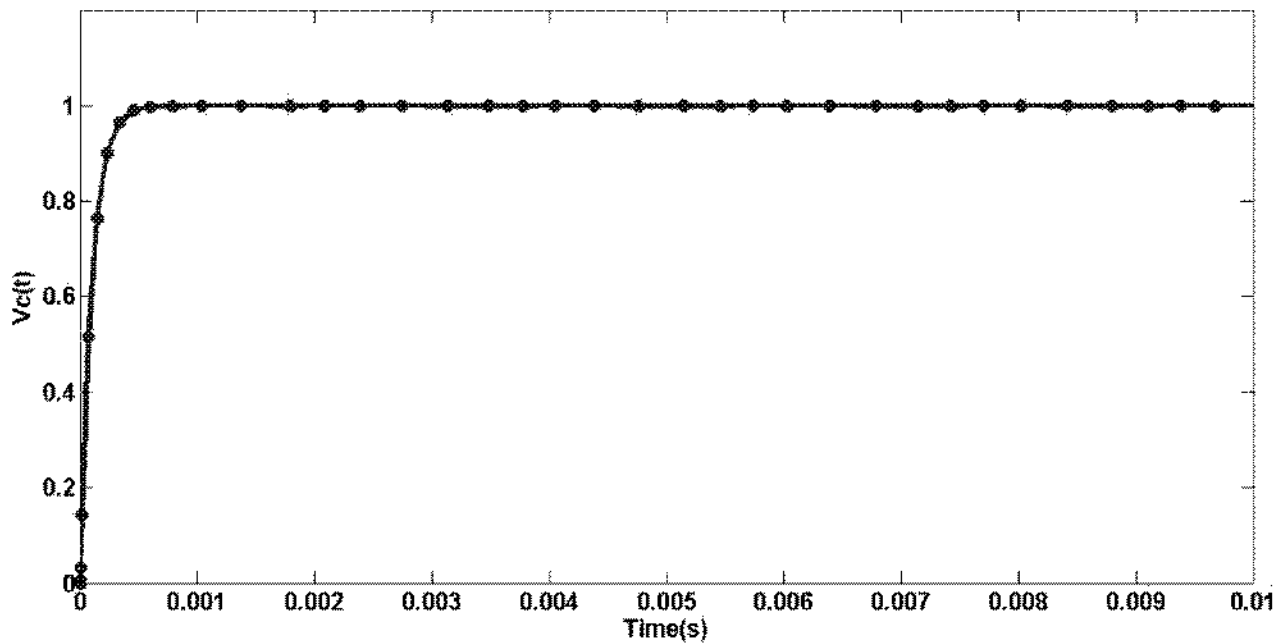

Ex $\Rightarrow$ RLC Circuit

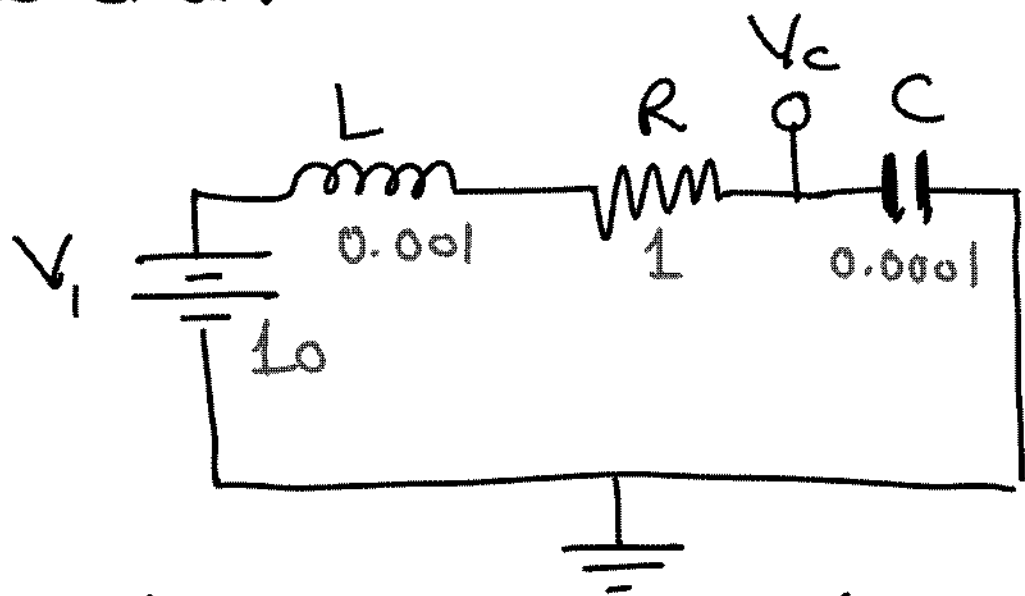use the SIMulink to solve the following RLC circuit



$$V_1(t) = L \frac{di(t)}{dt} + i(t) \times R + \frac{1}{C} \int i(t) dt$$

$\Downarrow$ take laplace

$$V_i = LS I + IR + \frac{I}{CS}$$

$$V_i = I \left(R + LS + \frac{1}{CS} \right) = \frac{LCs^2 + RCs + 1}{CS} \quad \text{①} \uparrow$$

$$V_c(t) = \frac{1}{C} \int i(t) dt$$

$$\Downarrow V_c = \frac{I}{CS} \rightarrow \text{②}$$

Divide ② by ①

$$\therefore \frac{V_c}{V_i} = \frac{1/CS}{(LCs^2 + RCs + 1)/CS}$$

$$\therefore \frac{V_c}{V_i} = \frac{1}{LCs^2 + RCs + 1}$$

$$\frac{V_c}{V_i} = \frac{1/LC}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

Assume $v_i = 10 u(t)$, $R=1$, $C=0.0001$, $L=0.001$

$$\frac{V_c}{V_i} = \frac{10,000,000}{s^2 + 1000s + 10000000}$$

↓
① Analytically

$$V_c = \frac{10^8}{s(s^2 + 1000s + 10^7)}$$

↓ partial fraction

$$\frac{10^8}{s(s^2 + 1000s + 10^7)} = \frac{10}{s} + \frac{As+B}{s^2 + 1000s + 10^7}$$

$$\downarrow 10^8 = 10(s^2 + 1000s + 10^7) + s(As+B)$$

Coefficient of $s = 0$

$$0 = 1000 + B \Rightarrow B = -1000$$

$$\text{Coefficient of } s^2 = 0 = 10 + A \Rightarrow A = -10$$

$$\therefore V_C = \frac{10}{s} - \frac{10s + 1000}{s^2 + 1000s + 10^7}$$




$$V_C = \frac{10}{s} - \frac{10(s+500) - 4000}{(s+500)^2 + 9750000}$$

$$V_C = \frac{10}{s} - 10 \frac{s+500}{(s+500)^2 + 9750000} + \frac{4000}{(s+500)^2 + 9750000}$$



inverse laplace
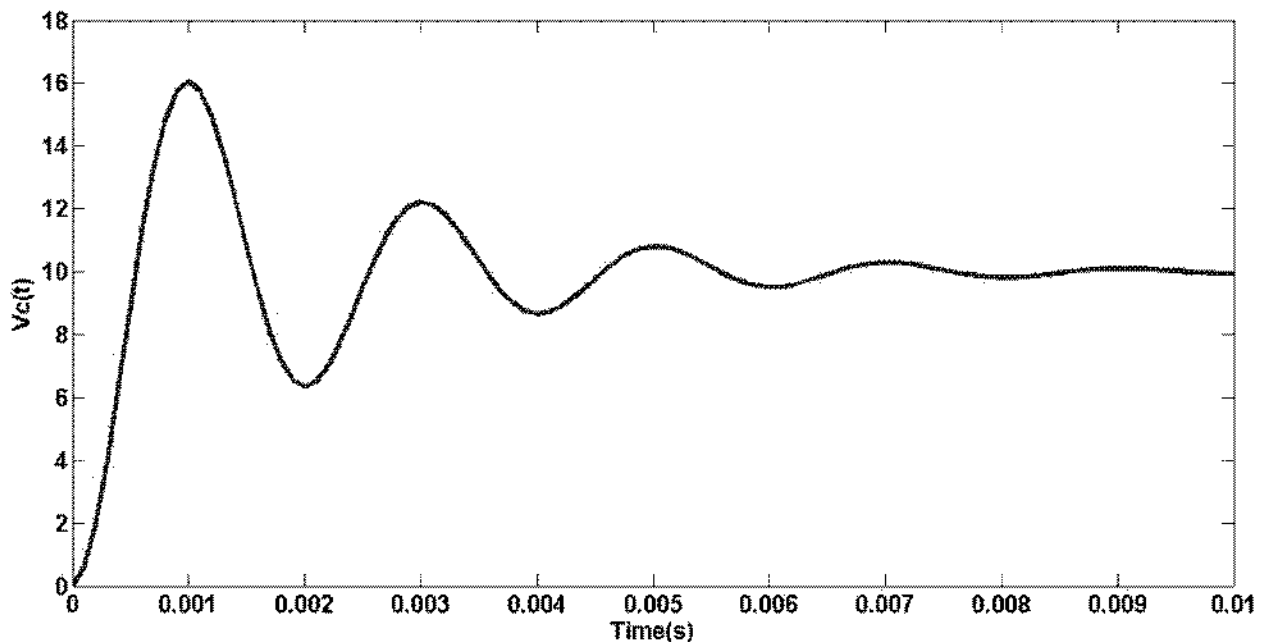
$$v_C(t) = 10 - 10 e^{-500t} \cos \sqrt{9750000} t - \frac{4000}{\sqrt{9750000}} e^{-500t} \sin \sqrt{9750000} t$$



② By MATLAB // .m file

$$\frac{V_c}{V_i} = \frac{1/LC}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$R = 1;$$

$$L = 0.001;$$

$$C = 0.0001;$$

$$\text{num} = 1/(L \times C);$$


$$\text{den} = [1 \quad R/L \quad 1/(L \times C)];$$

$$\text{sys} = \text{tf}(\text{num}, \text{den});$$

$$t = 0:0.0001:0.01;$$

$$V_c = \text{step}(10 \times \text{sys}, t)$$



$$\text{plot}(t, V_c)$$

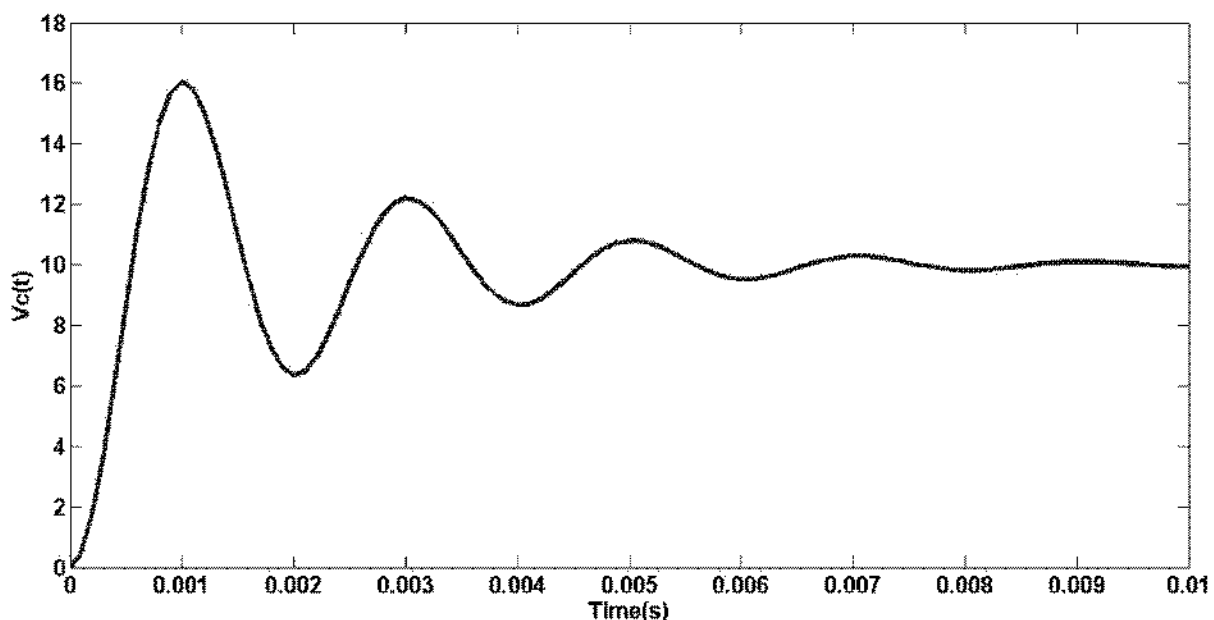


③ By Simulink

$$\frac{V_c}{V_i} = \frac{1/LC}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$V_c'' + \frac{R}{L} V_c' + \frac{1}{LC} V_c = \frac{1}{LC} V_i$$

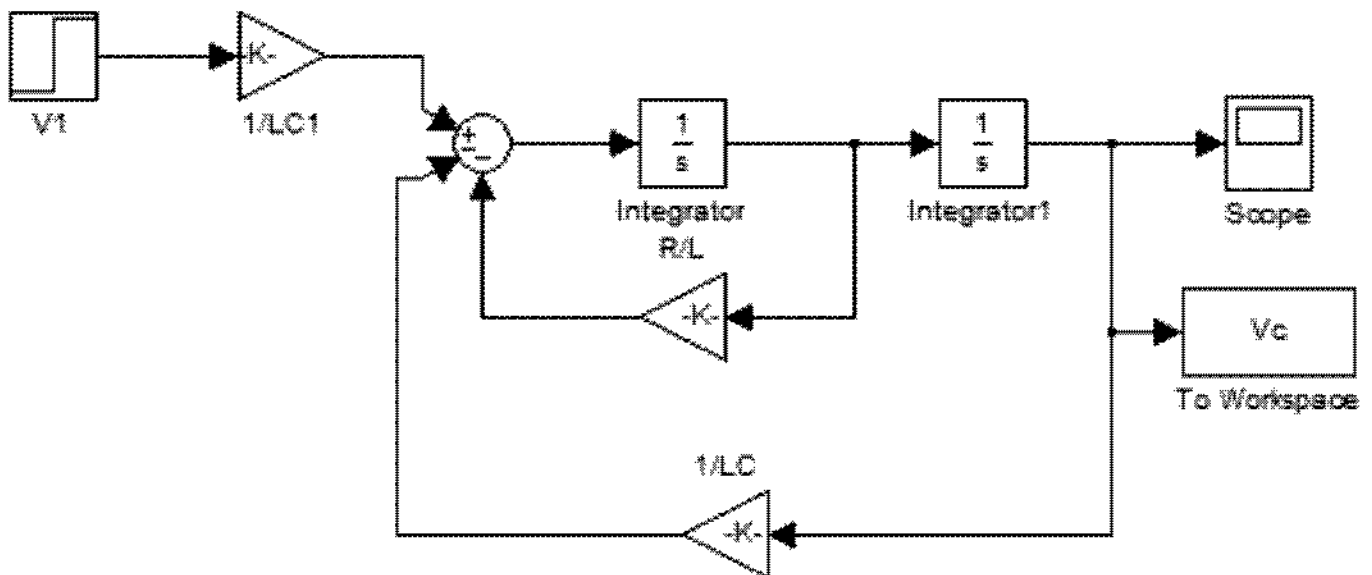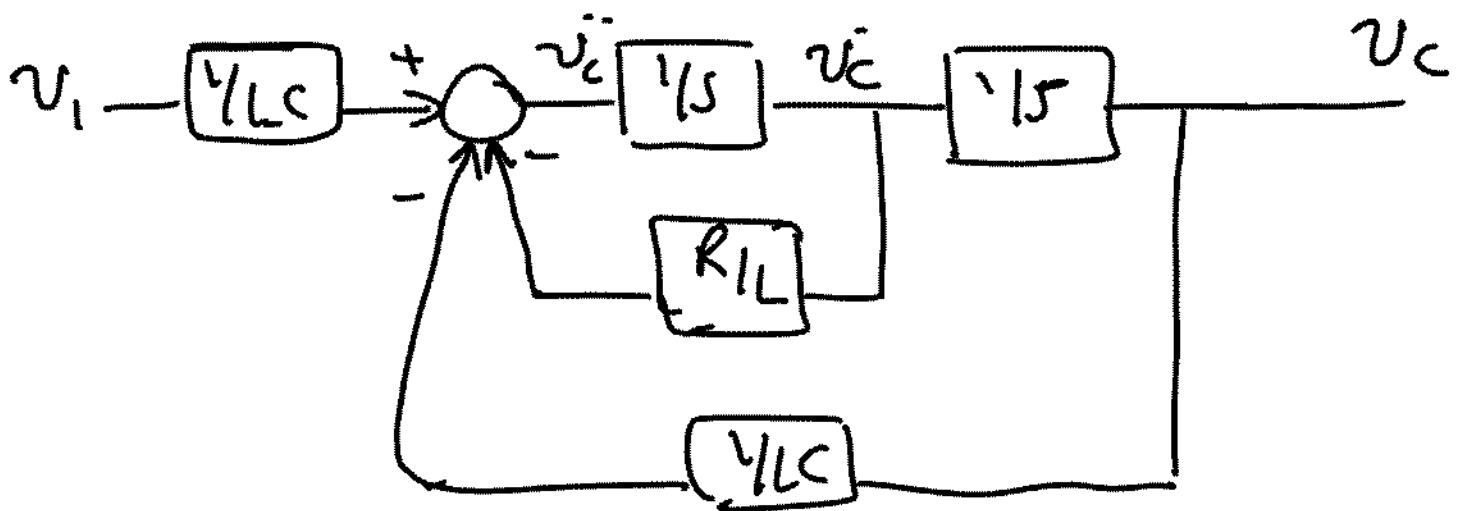


Report 00

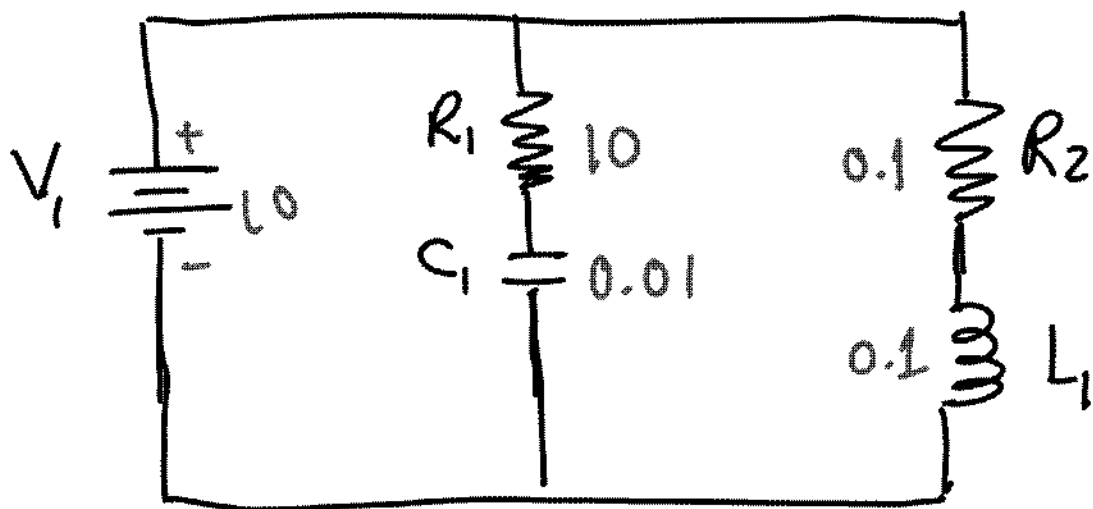


operational amplifier $\Rightarrow$

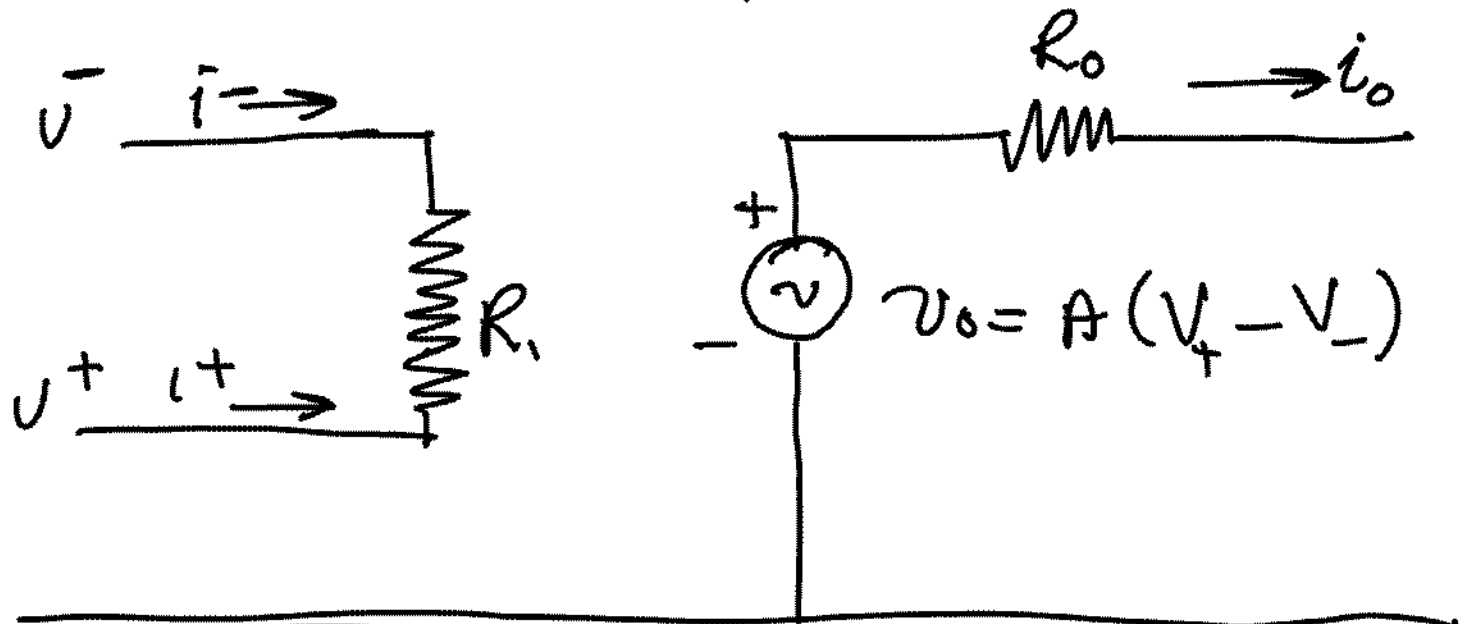the simplified circuit of the op-amp is shown



schematic symbol

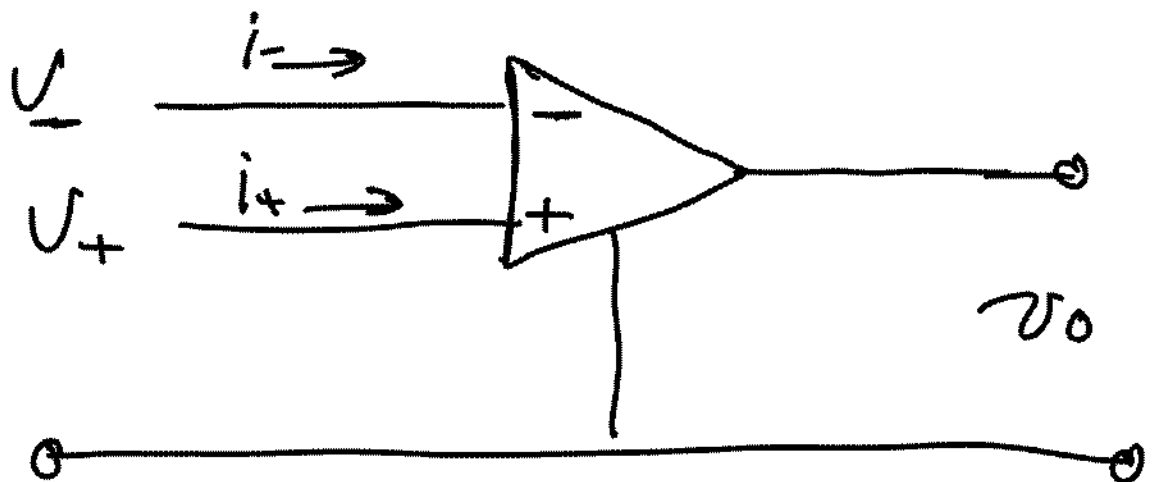

if the positive terminal is not shown, it is assumed to be connected to ground, $V_+ = 0$



And the reduced symbol below is used,




it is usually assumed that the op-amp is ideal with the values $R_i = \infty$, $R_o = 0$, $A = \infty$

so ① $I_+ = I_- = 0$

② $V_+ = V_-$

Ex

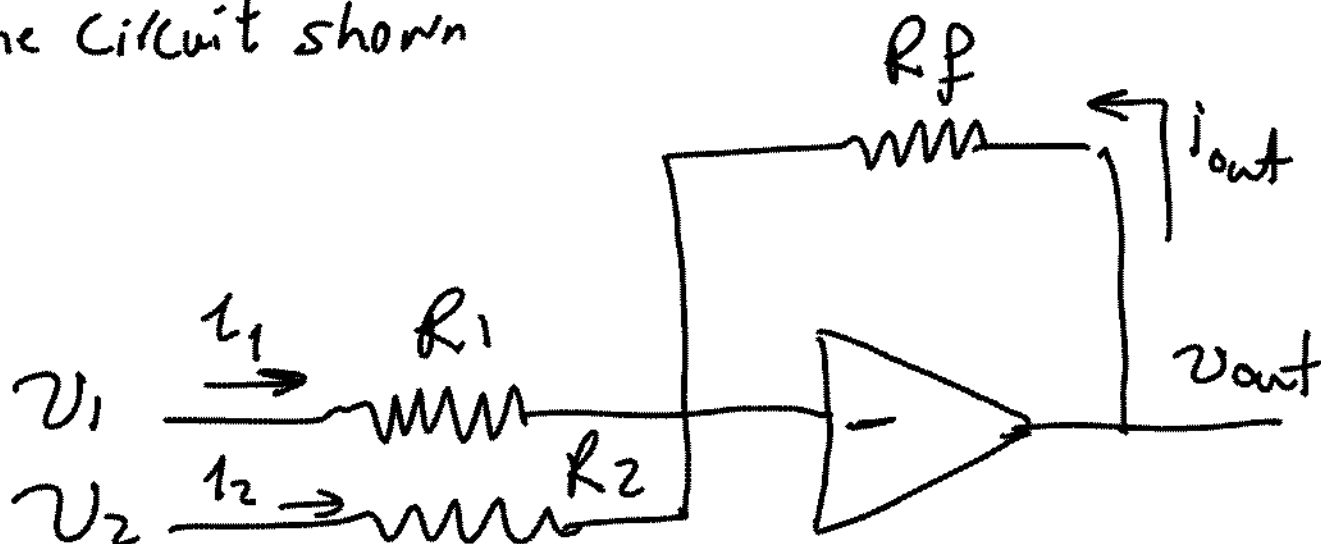find the equations and transfer function of the circuit shown



$$\therefore V_+ = 0 \Rightarrow V_- = 0$$

$$I_1 = \frac{V_1}{R_1}, \quad I_2 = \frac{V_2}{R_2}, \quad I_{out} = \frac{V_{out}}{R_f}$$

$$I_1 + I_2 + I_3 = 0$$

$$\Downarrow \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_{out}}{R_f} = 0$$

$$\therefore V_{out} = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 \right]$$

the circuit o/p is a weighted sum of the input voltages with a sign change.



Summer circuit

Ex $\Rightarrow$ Integrator



$$\text{so } v_+ = 0 \Rightarrow v_- = 0$$

$$\frac{v_{in}}{R_{in}} + C \frac{dv_{out}}{dt} = 0$$

$$\text{so } \frac{dv_{out}}{dt} = - \frac{v_{in}}{CR_{in}}$$

$$\text{so } v_{out} = \frac{-1}{R_{in}C} \int_0^t v_{in}(\tau) d\tau + v_{out}(0)$$

(or)


$$sV_{out} = \frac{-1}{R_{in}C} V_{in}$$

$$\text{so } \frac{V_{out}}{V_{in}} = \frac{-1}{sR_{in}C}$$

Prob.

Do it again assuming $u(t) = t$

Ex $\Rightarrow$

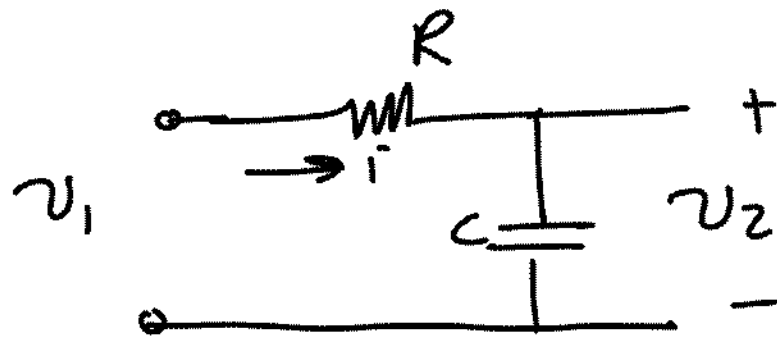

$$v_1(t) = i(t)R + \frac{1}{C} \int i(t) dt$$

$$v_2(t) = \frac{1}{C} \int i(t) dt$$


$\Downarrow$

$$V_1 = IR + \frac{I}{Cs} = I \left(R + \frac{1}{Cs} \right)$$

$$V_2 = I/Cs$$

$$\frac{V_2}{V_1} = \frac{1/Cs}{R + 1/Cs} = \frac{1}{1 + RCs}$$

Ex $\Rightarrow$

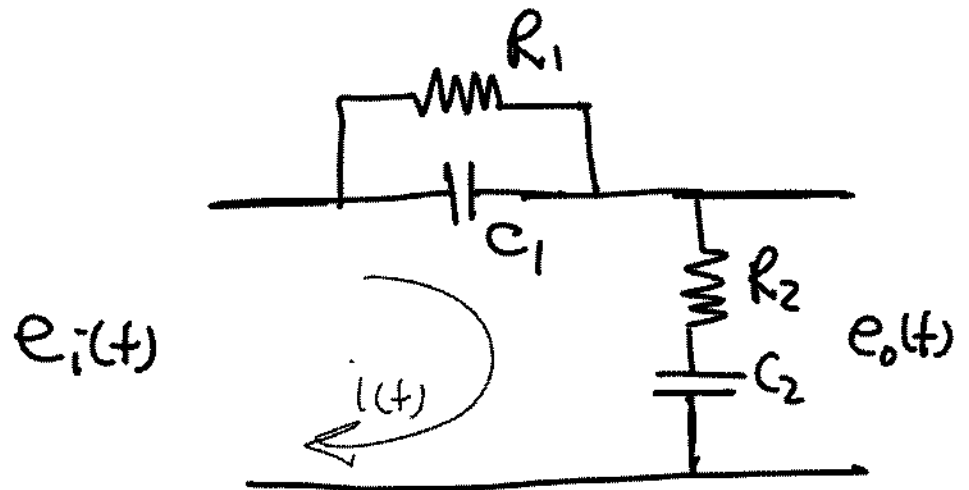

$$Z_1 = \frac{R_1 / sC_1}{R_1 + 1/sC_1}$$

$$= \frac{R_1}{1 + sC_1 R_1}$$

$$Z_2 = R_2 + 1/sC_2 = \frac{1 + sC_2 R_2}{sC_2}$$

$$E_i = I(s) \left[\frac{R_1}{1 + sC_1 R_1} + \frac{1 + sC_2 R_2}{sC_2} \right]$$

$$E_i = I(s) \left[\frac{SC_2 R_1 + (1 + SC_2 R_2)(1 + SC_1 R_1)}{SC_2 (1 + SC_1 R_1)} \right]$$

$$E_o = I(\omega) \left(\frac{1 + SC_2 R_2}{SC_2} \right)$$

$$\therefore \frac{E_o}{E_i} = \frac{(1 + SC_1 R_1)(1 + SC_2 R_2)}{SC_2 R_1 + (1 + SC_2 R_2)(1 + SC_1 R_1)}$$


DC-Motor

$$\text{Torque} \propto \bar{I}_a \bar{I}_f$$

① Field Control

I_a : Constant


$$T \propto I_f$$

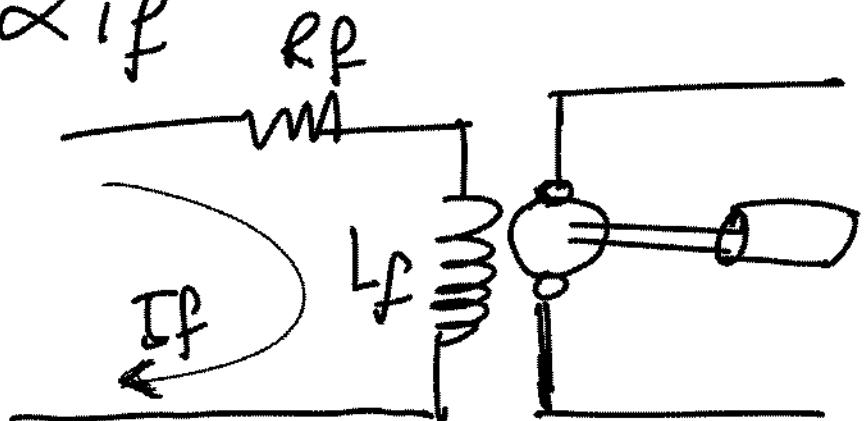

$$V_f = I_f (R_f + sL_f)$$


$$T = k I_f$$

$$T = (Is^2 + bs) \Theta$$

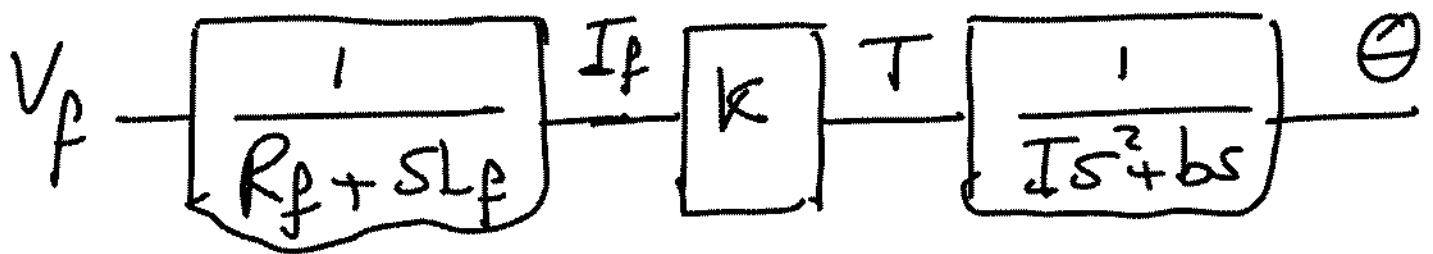

$$\Theta/V_f = \frac{k}{(R_f + sL_f)(Is^2 + bs)}$$

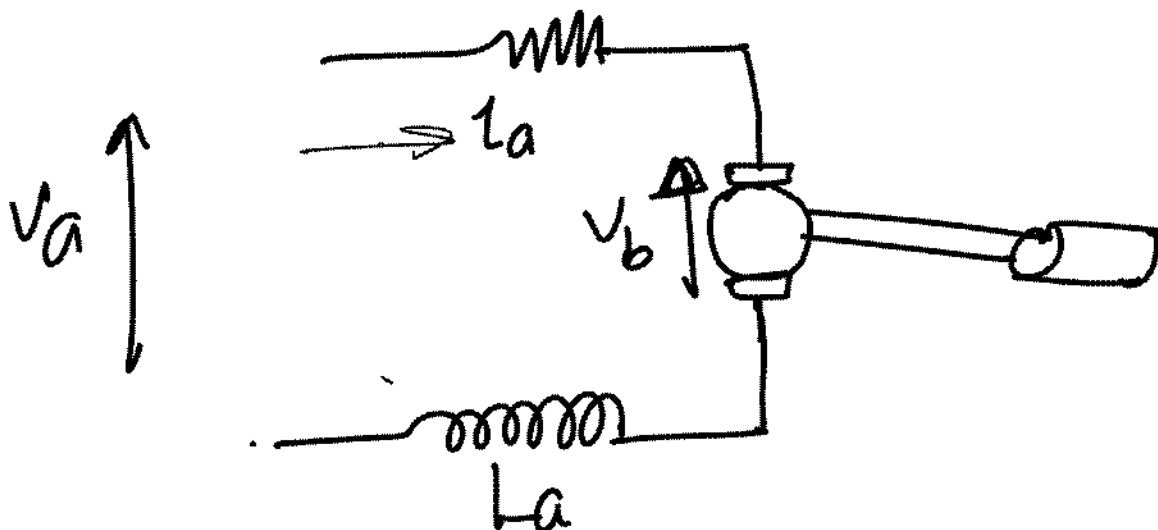② Armature Control I_f : Constant
 $T \propto I_a$




$$V_a - V_b = I_a (R + sL_a)$$

$$V_b \propto \dot{\theta}$$


$$V_b = k_b s \theta$$

$$T = k I_a$$

$$T = (Js^2 + bs)\theta$$

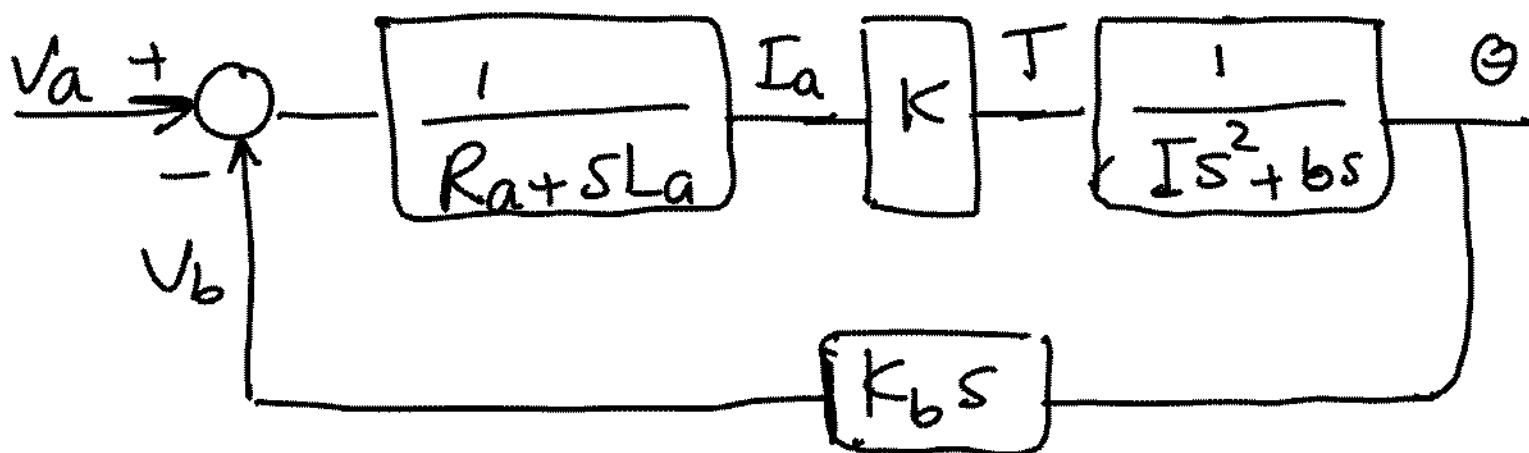

Ex $\Rightarrow$

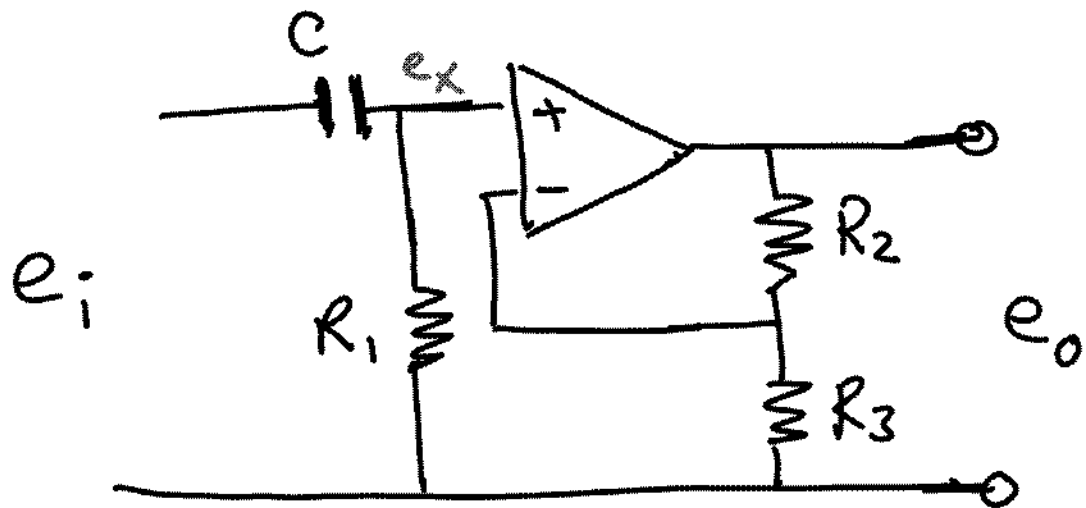

find E_o/E_i

Sol $\Rightarrow$


$$\frac{E_x}{E_i} = \frac{R_1}{R_1 + 1/sC}$$

$$\frac{E_x}{E_o} = \frac{R_3}{R_2 + R_3}$$

$$\frac{E_o}{E_i} = \frac{R_1}{1/sC + R_1} * \frac{R_3 + R_2}{R_3}$$

$$= \frac{R_1 (R_3 + R_2)}{R_3 (R_1 + 1/sC)}$$

Prob.

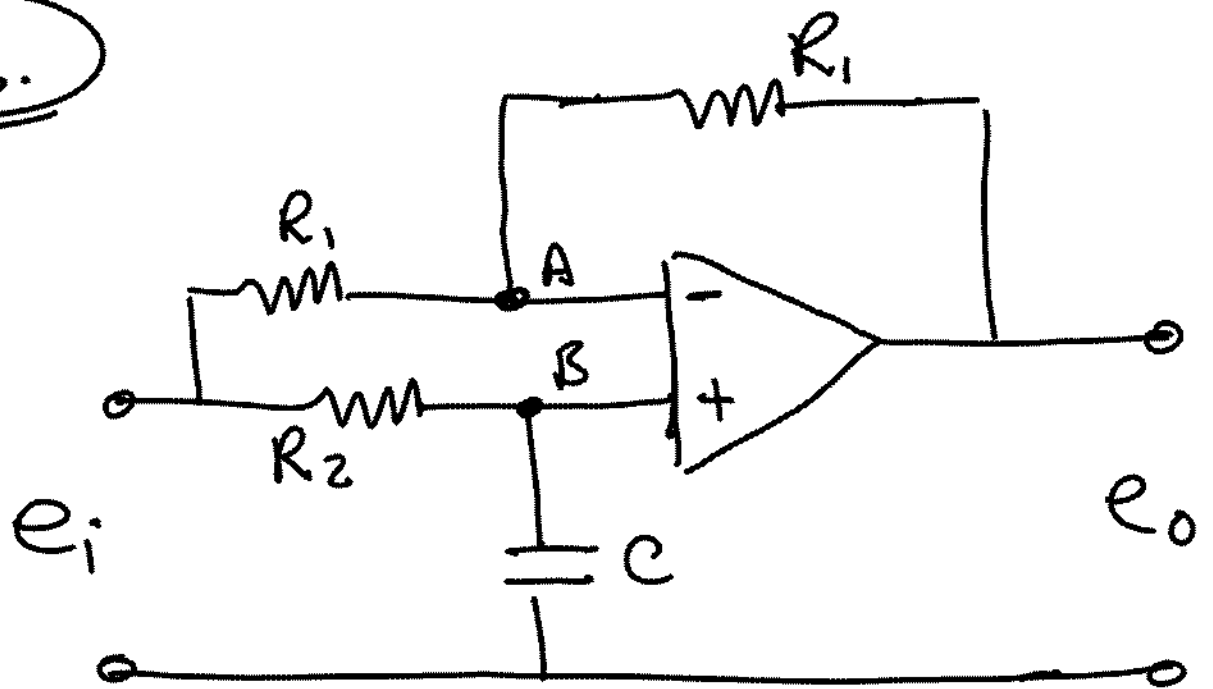

Find E_o / E_i