



Question-1 (10 Points)

A. A 16-bit register contains the following: 0111100101000101 Interpret the contents as:

- BCD number $\rightarrow$ 7945
- Binary number $\rightarrow$ 0111 1001 0100 0101

B. Simplify the following Boolean equation using Boolean theorems

$$Y = \bar{A}\bar{B} + \bar{A}B\bar{C} + (\bar{A} + \bar{C})$$

$$= \bar{A}\bar{B} + \bar{A}B\bar{C} + \bar{A}C$$

$$= \bar{A}(\bar{B} + B\bar{C}) + \bar{A}C = \bar{A}(\bar{B} + B)(\bar{B} + \bar{C}) + \bar{A}C$$

$$= \bar{A}\bar{B} + \bar{A}C + \bar{A}C = \bar{A}\bar{B} + \bar{A}(C + \bar{C})$$

$$= \bar{A}\bar{B} + \bar{A} = \bar{A}(\bar{B} + 1) = \bar{A}$$

C. Find the sum-of-product function of

$$f(w, x, y, z) = wy + \bar{x}z + \bar{w}y\bar{z}$$

$$= \sum (1, 2, 3, 6, 9, 10, 11, 14, 15)$$

$$= \bar{w}\bar{x}\bar{y}z + \bar{w}\bar{x}y\bar{z} + \bar{w}\bar{x}yz + \bar{w}x\bar{y}\bar{z} + w\bar{x}\bar{y}z + w\bar{x}y\bar{z} + w\bar{x}yz + wx\bar{y}\bar{z} + wxyz$$

Question-2 (10 Points)

A. Simplify the Boolean function F together with the don't care conditions d in (1) sum-of-products form



$$F(w, x, y, z) = \sum (0, 1, 2, 3, 7, 8, 10)$$

$$d(w, x, y, z) = \sum (5, 6, 11, 15)$$

$$F = \bar{x}\bar{z} + \bar{w}z$$

w\y\z	00	01	11	10
00	1	1	1	1
01		X	1	X
11			X	
10	1		X	1

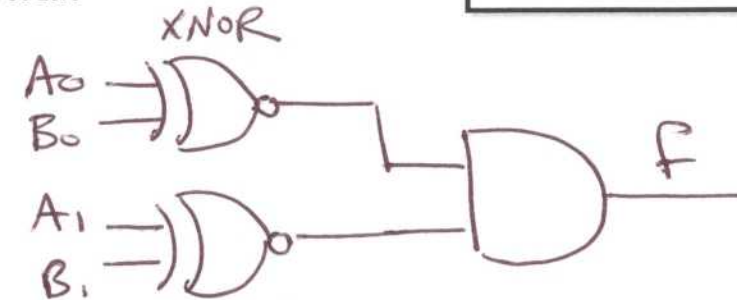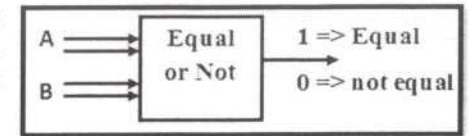B. Design a circuit to perform the comparison between two 2-bit numbers, if they are equal, the output will be one, otherwise the output will be zero



A, A ₀	B, B ₀	00	01	11	10
00		1			
01			1		
11				1	
10					1


$$F = \bar{A}_1\bar{A}_0\bar{B}_1\bar{B}_0 + \bar{A}_1A_0\bar{B}_1B_0 + A_1A_0B_1B_0 + A_1\bar{A}_0B_1\bar{B}_0$$

Question-3 (10 Points)

A. Find the expression for the Boolean function Y

$$Y = A\bar{B} + \bar{B}\bar{C}$$

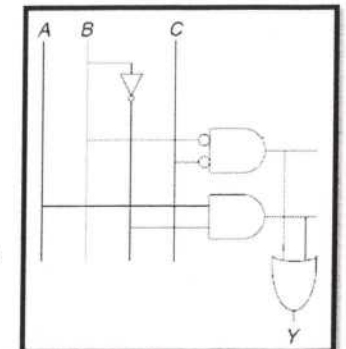B. Two 2-bit numbers are to be added. Design a circuit with the two numbers as inputs and their sum is the output



Q3-B

$A_1 A_0$	$B_1 B_0$	C_2	C_1	C_0
00	00	0	0	0
00	01	0	0	1
00	10	0	1	0
00	11	0	1	1
01	00	0	0	1
01	01	0	1	0
01	10	0	1	1
01	11	1	0	0
10	00	0	1	0
10	01	0	1	1
10	10	1	0	0
10	11	1	0	1
11	00	0	1	1
11	01	1	0	0
11	10	1	0	1
11	11	1	1	0

$A_1 A_0 \backslash B_1 B_0$	00	01	11	10
00				
01			1	
11		1	1	1
10			1	1

$$\Rightarrow C_2 = A_1 B_1 + A_0 B_1 B_0$$

$A_1 A_0 \backslash B_1 B_0$	00	01	11	10
00			1	1
01		1		1
11	1		1	
10	1	1		

$$\Rightarrow C_1 = \bar{A}_1 \bar{A}_0 B_1 + \bar{A}_1 B_1 \bar{B}_0 + A_1 \bar{A}_0 \bar{B}_1 + A_1 \bar{B}_1 \bar{B}_0 + \bar{A}_1 \bar{A}_0 \bar{B}_1 B_0 + A_1 A_0 B_1 B_0$$

$A_1 A_0 \backslash B_1 B_0$	00	01	11	10
00		1	1	
01	1			1
11	1			1
10		1	1	

$$C_0 = A_0 \bar{B}_0 + \bar{A}_0 B_1$$