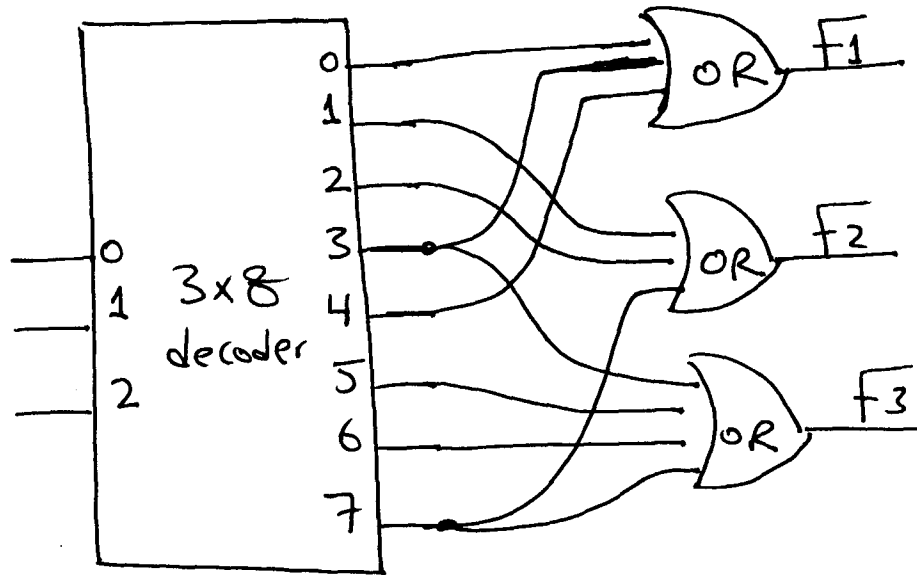


Question-1 (20 Points)

A. A combinational circuit is specified by the following three Boolean functions:

$$F_1 = \sum(0,3,4) \quad F_2 = \sum(1,2,7) \quad F_3 = \prod(0,1,2,4)$$

Implement the circuit with a **decoder** and **external OR gate**



Implement the following Boolean function $F(A, B, C, D) = \sum(0,3,5,6,9,10,11)$ with 4×1 Multiplexer (Do not use 8×1 MUX)


A	B	C	D	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

$$F = C \odot D$$

$$F = C \oplus D$$


$$F = C + D$$

$$F = 0$$

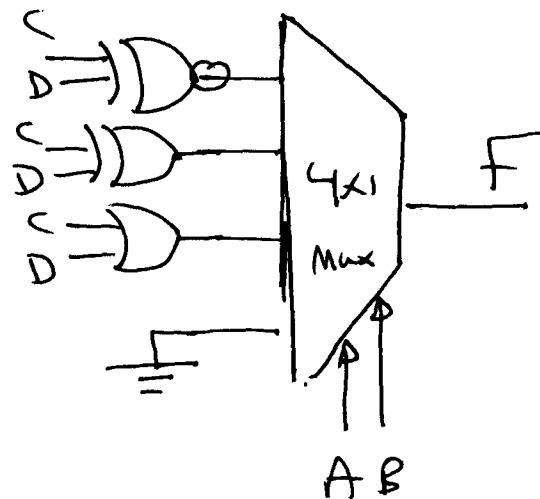

11/11/17

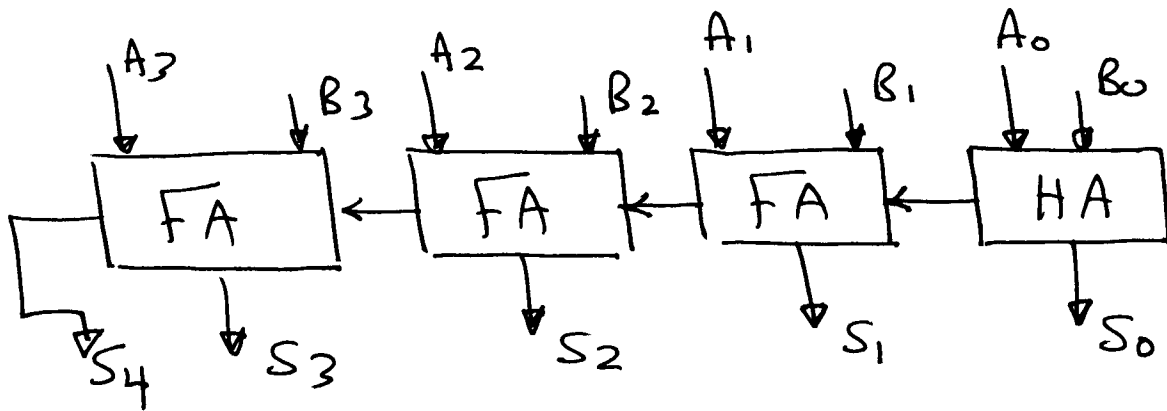C. Design a 4-bit binary parallel adder using only half adder and full adder



D. Design a logic circuit that computes the function $f(x) = x^2 - x + 2$ for a 2-bit number x


x_1	x_0	f_3	f_2	f_1	f_0
0	0	0	0	1	0
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

$$f_0 = 0$$

$$f_1 = \overline{x_1}$$


$$f_2 = x_1 \overline{x_0}$$

$$f_3 = x_1 x_0$$

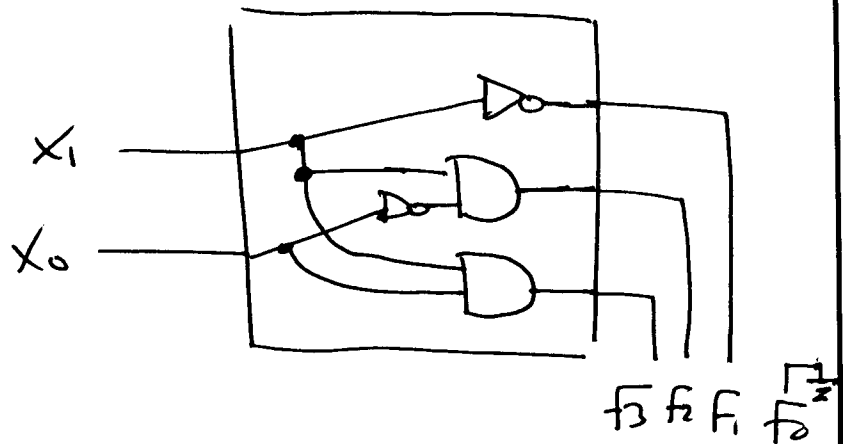


Question-2 (10 Points)

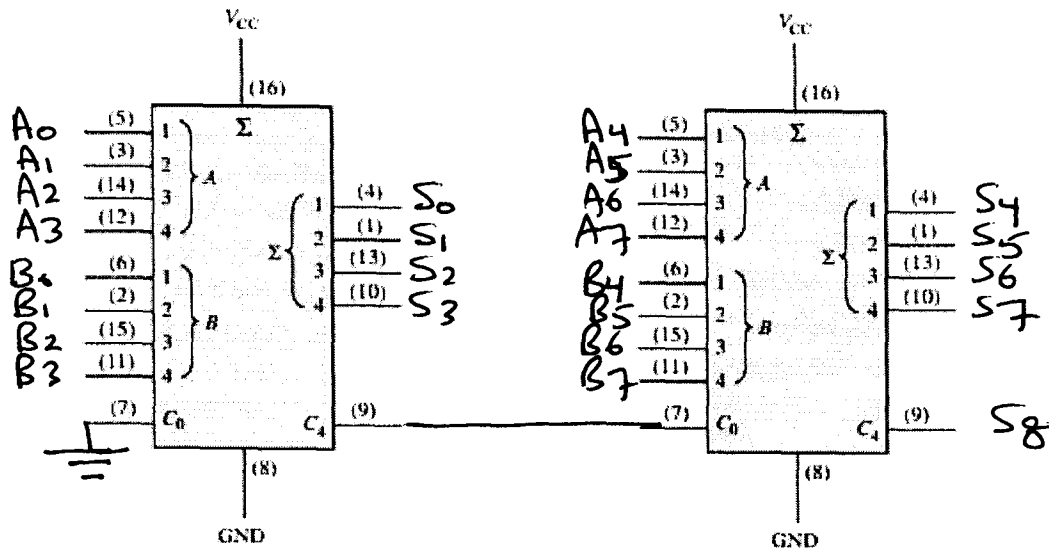A. Show how two 74HC283 adders can be connected to form an 8-bit parallel adder.



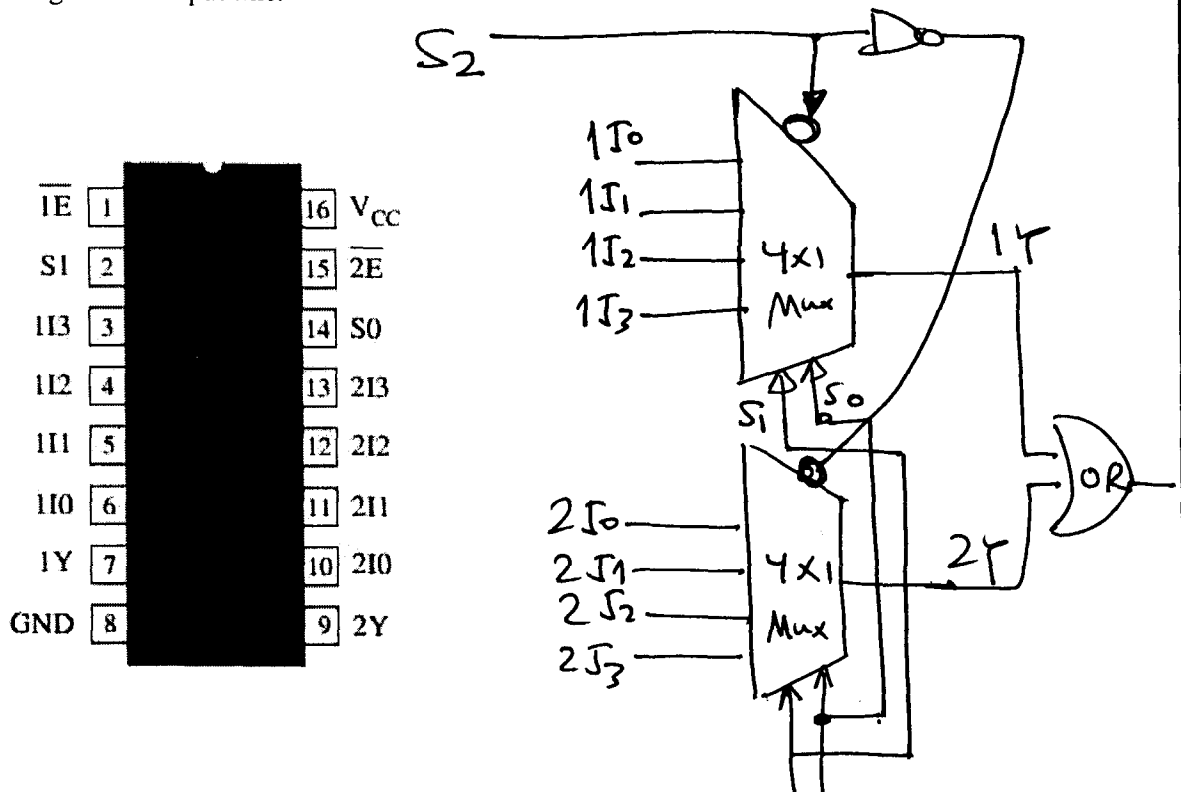
B. Use The 74HC153 dual four-input data selector/multiplexer and any other logic necessary to multiplex 8 data lines onto a single data-output line.



Question-3 (20 Points)

A. Design a digital circuit that can output the maximum number between two 4-bit numbers A and B

Hint: output = $\max(A, B)$

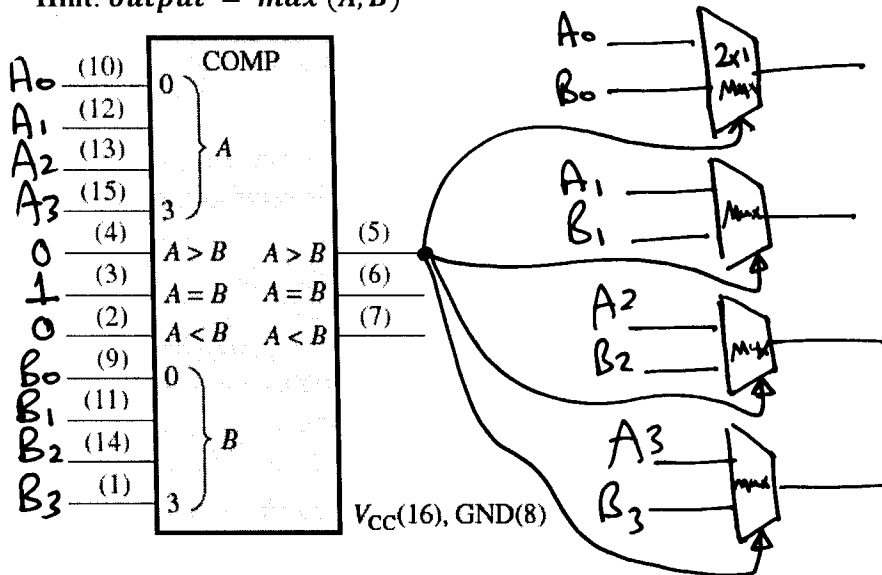

B. Use Karnaugh map to obtain minimized SOP for the following function

Hint: d: do not care



$$F(A, B, C) = \sum(1, 3, 5, 7) \quad d(A, B, C) = \sum(4, 6)$$

$$F = C$$

A \ BC	00	01	11	10
0		1	1	
1	X	1	1	X

C. Implement the function F represented by the logic diagram shown next by using decoder

$$F = \sum(3, 4, 5, 6, 7)$$

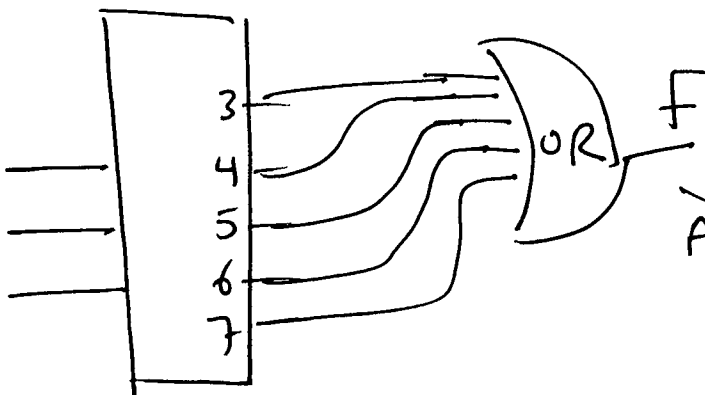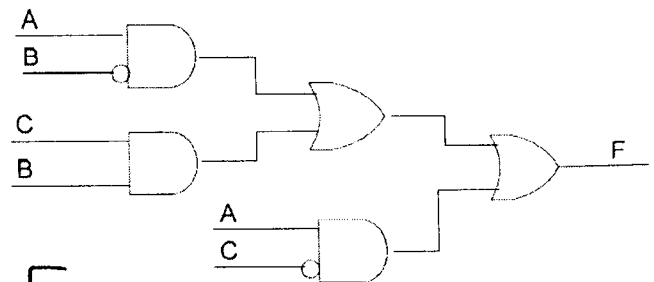

$$F = A\bar{B} + CB + A\bar{C}$$

A \ BC	00	01	11	10
0			1	
1	1	1	1	1