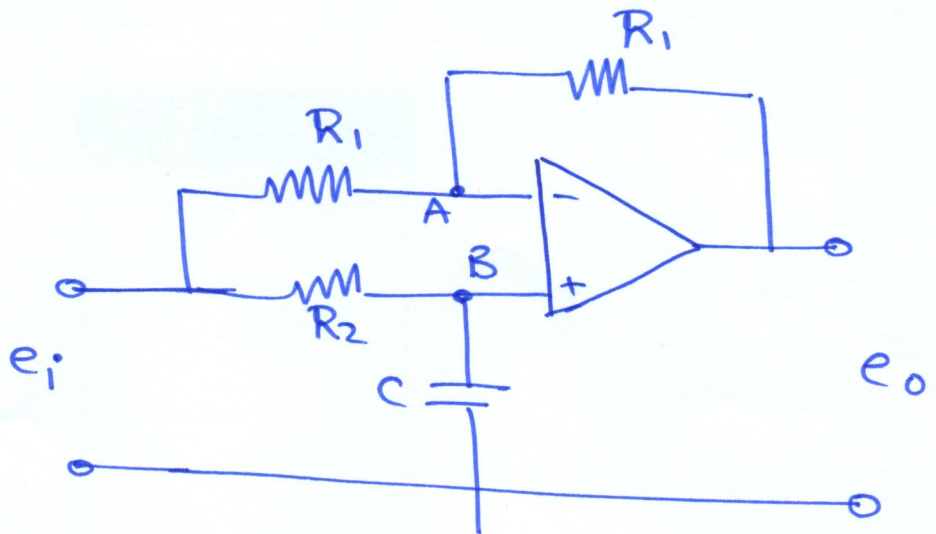


Find $\frac{E_o(s)}{E_i(s)}$

Sol.

$$E_A = E_B$$



$$\frac{E_i - E_A}{R_1} = \frac{E_A - E_o}{R_1}$$

$$\therefore E_i - E_A = E_A - E_o$$

$$E_A = \frac{1}{2} (E_i + E_o)$$

$$E_B = E_i \times \frac{1/sC}{R_2 + 1/sC}$$

$$= E_i \frac{1}{R_2 C s + 1}$$

$$\therefore E_A = E_B$$


$$\therefore \frac{1}{2} (E_i + E_o) = E_i \frac{1}{R_2 C s + 1}$$

$$E_o = E_i \left(\frac{2}{R_2 C s + 1} - 1 \right)$$

$$E_o = E_i \left(\frac{1 - R_2 C s}{1 + R_2 C s} \right) \Rightarrow \frac{E_o}{E_i} = \frac{s - \frac{1}{R_2 C}}{s + \frac{1}{R_2 C}}$$

Find $\frac{E_o(s)}{E_i(s)}$

Sol.

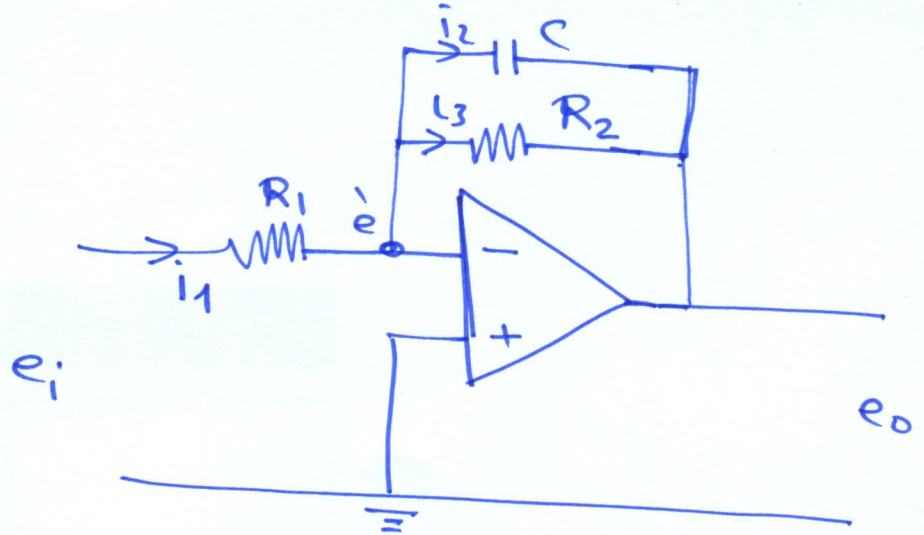

$$\therefore V^- = V^+$$

$$\therefore V^+ = 0$$

$$\therefore V^- = 0$$

$$\therefore V^- = e^- = 0$$

$$\therefore i_1 = i_2 + i_3$$


$$\frac{E_i}{R_1} = -\frac{E_o}{R_2} - CS E_o$$

$$\frac{E_i}{R_1} = -E_o \left(\frac{1}{R_2} + CS \right) = -E_o \left(\frac{1 + CR_2 S}{R_2} \right)$$

$$\therefore \frac{E_o}{E_i} = \frac{-R_2}{R_1} \frac{1}{1 + R_2 CS}$$

Prob. Find $\frac{E_o(s)}{E_i(s)}$

Sol.

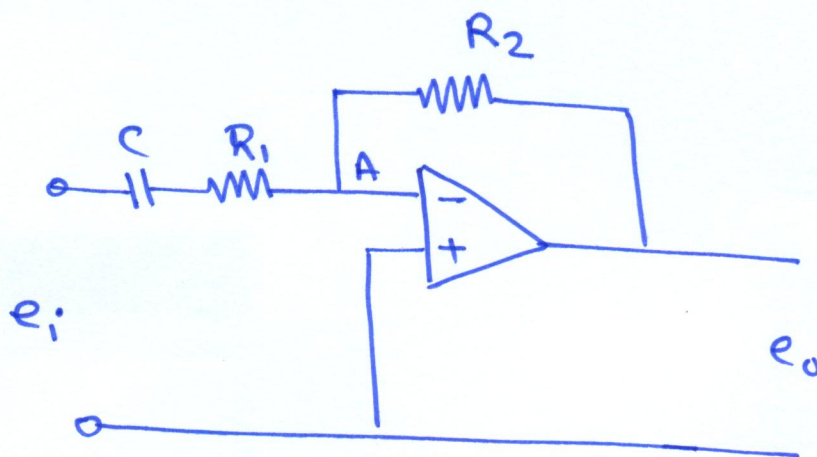

$$E_A = 0$$

$$\frac{E_i - E_A}{R_1 + 1/sC} = \frac{E_A - E_o}{R_2}$$

$$\therefore E_A = 0$$

$$\therefore \frac{E_i}{R_1 + 1/sC} = \frac{-E_o}{R_2}$$

$$\therefore \frac{E_o}{E_i} = \frac{-R_2}{R_1 + 1/sC} = \frac{-R_2 C s}{1 + R_1 C s}$$

Prob.

Find $\frac{E_o}{E_i}$

Sol.

$$E_A = E_B$$


$$E_A = E_i \frac{R_1}{R_1 + 1/sC} = E_i \frac{R_1 C s}{1 + R_1 C s}$$

$$E_B = E_o \frac{R_3}{R_2 + R_3}$$

$$\therefore E_i \frac{R_1 C s}{1 + R_1 C s} = E_o \frac{R_3}{R_2 + R_3}$$

$$\therefore \frac{E_o}{E_i} = \frac{R_1 C s}{1 + R_1 C s} \times \frac{R_2 + R_3}{R_3}$$
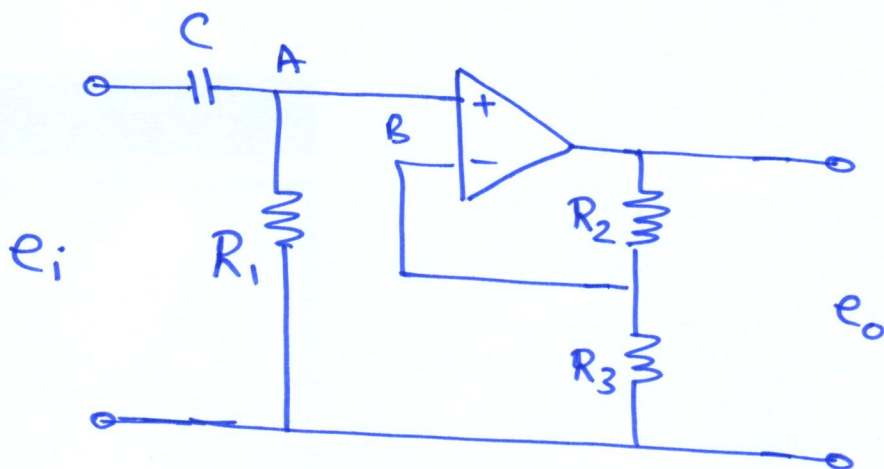
$$\frac{E_o}{E_i} = \frac{R_1 (R_2 + R_3)}{R_3} \times \frac{C s}{1 + R_1 C s}$$




Prob.

A first step toward a realistic model of an op-amp is given by the following equations and is shown in fig. below

$$V_{out} = \frac{10^7}{s+3} (V_+ - V_-)$$

$$I_+ = I_- = 0$$

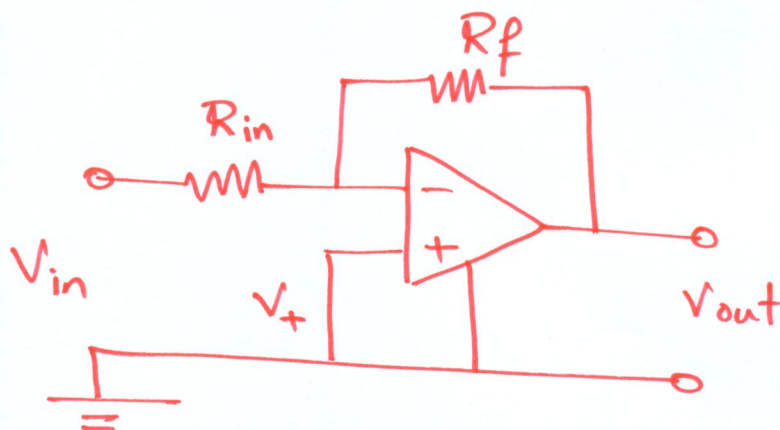Find the transfer function of the simple amplification circuit shown using this model



Sol.

$$\frac{V_{in} - V_-}{R_{in}} = \frac{V_- - V_{out}}{R_f}$$

$$V_{in} - V_- = \frac{R_{in}}{R_f} (V_- - V_{out})$$

$$V_{in} + \frac{R_{in}}{R_f} V_{out} = V_- \left(\frac{R_{in}}{R_f} + 1 \right)$$

$$= V_- \left(\frac{R_{in} + R_f}{R_f} \right)$$

$$\therefore V_- = \frac{R_f}{(R_{in} + R_f)} \times \left(V_{in} + \frac{R_{in}}{R_f} V_{out} \right)$$

$$\therefore V_- = \left(\frac{R_f}{R_{in} + R_f} \right) \times \left(V_{in} + \frac{R_{in}}{R_f} V_{out} \right)$$

$$V_- = \frac{R_f}{R_{in} + R_f} V_{in} + \frac{R_{in}}{R_{in} + R_f} V_{out}$$

$$\therefore V_{out} = \frac{10^7}{s+3} (V_+ - V_-)$$

$$\therefore V_+ = 0$$


$$\therefore V_{out} = -\frac{10^7}{s+3} \left(\frac{R_f}{R_{in} + R_f} V_{in} + \frac{R_{in}}{R_{in} + R_f} V_{out} \right)$$

$$V_{out} \left(1 + \frac{10^7}{s+3} \times \frac{R_{in}}{R_{in} + R_f} \right) = \frac{-10^7}{s+3} \frac{R_f}{R_{in} + R_f} V_{in}$$

$$V_{out} \left(\frac{(s+3)(R_{in} + R_f) + 10^7 R_{in}}{(s+3)(R_{in} + R_f)} \right) = \frac{-10^7 R_f}{(s+3)(R_{in} + R_f)} V_{in}$$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{-10^7 R_f}{(s+3)(R_{in} + R_f) + 10^7 R_{in}}$$

Prob.

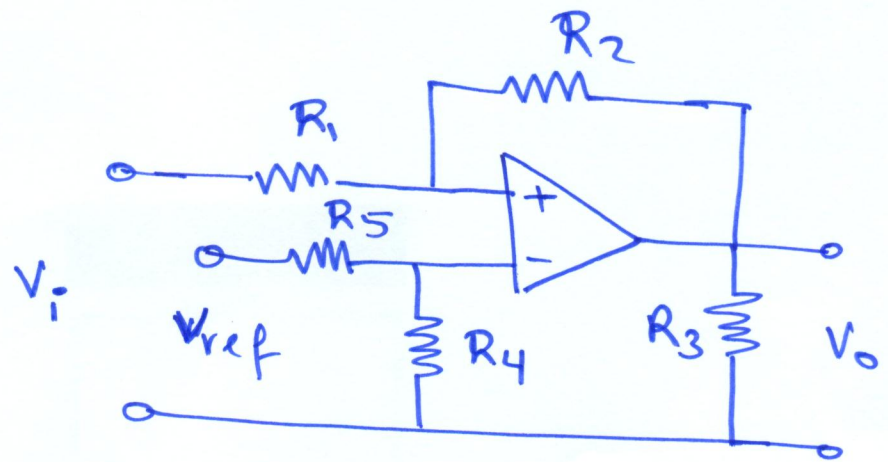

$$\frac{V_i - V^+}{R_1} = \frac{V^+ - V_o}{R_2} = \frac{V_o}{R_3}$$

$$\frac{V_i - V^+}{R_1} = \frac{V^+ - V_o}{R_2}$$

$$V_i - V^+ = \frac{R_1}{R_2} (V^+ - V_o)$$

$$\begin{aligned} \left(V_i + \frac{R_1}{R_2} V_o \right) &= V^+ \left(\frac{R_1}{R_2} + 1 \right) \\ &= V^+ \frac{R_1 + R_2}{R_2} \end{aligned}$$

$$\therefore V^+ = \frac{R_2}{R_1 + R_2} V_{in} + \frac{R_1}{R_1 + R_2} V_o$$

$$\therefore V^- = V_{ref} \frac{R_4}{R_4 + R_5}$$

$$\therefore V_{ref} \frac{R_4}{R_4 + R_5} = \frac{R_2}{R_1 + R_2} V_{in} + \frac{R_1}{R_1 + R_2} V_o$$

$$\therefore V_o = -\frac{R_2}{R_1} V_{in} + \frac{R_4(R_1 + R_2)}{R_1(R_4 + R_5)} V_{ref}$$